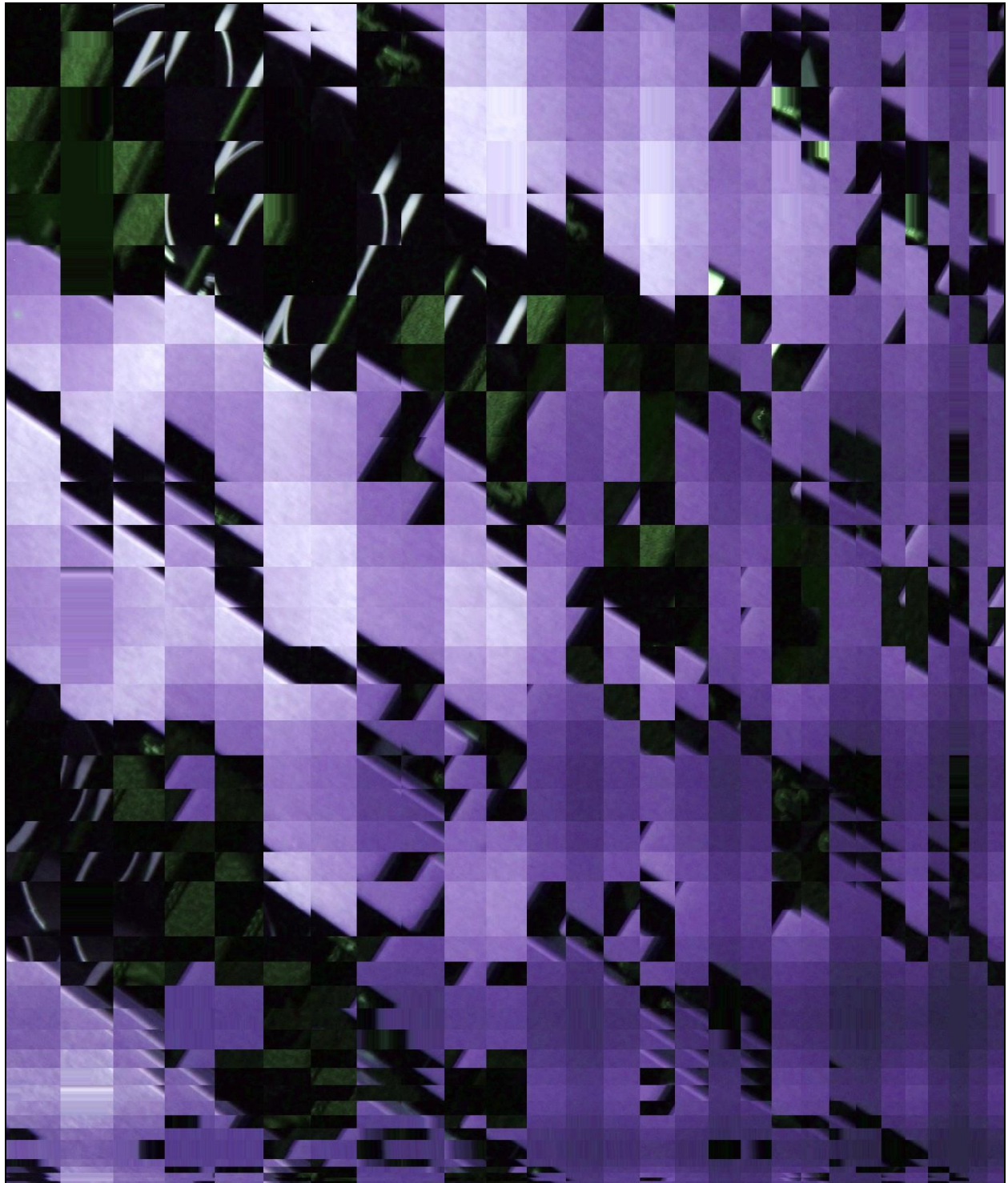


# DC Electrical Circuits

## Laboratory Manual



James M. Fiore



# Laboratory Manual for DC Electrical Circuits

by

James M. Fiore

Version 1.0.4, 30 August 2016

This **Laboratory Manual for DC Electrical Circuits**, by **James M. Fiore** is copyrighted under the terms of a Creative Commons license:



This work is freely redistributable for non-commercial use, share-alike with attribution

Published by James M. Fiore via dissidents

For more information or feedback, contact:

James Fiore, Professor  
Electrical Engineering Technology  
Mohawk Valley Community College  
1101 Sherman Drive  
Utica, NY 13501  
[jfiore@mvcc.edu](mailto:jfiore@mvcc.edu)

or via [www.dissidents.com](http://www.dissidents.com)

Cover art, *Vibralt II*, by the author

# Introduction

This manual is intended for use in a DC electrical circuits course and is appropriate for two and four year electrical engineering technology curriculums. The manual contains sufficient exercises for a typical 15 week course using a two to three hour practicum period. The topics range from basic laboratory procedures and resistor identification through series-parallel circuits, mesh and nodal analysis, superposition, Thevenin's Theorem, Maximum Power Transfer Theorem, and concludes with an introduction to capacitors and inductors. For equipment, each lab station should include a dual adjustable DC power supply and a quality DMM capable of reading DC voltage, current and resistance. A selection of standard value  $\frac{1}{4}$  watt carbon film resistors ranging from a few ohms to a few mega ohms is required along with 10 k $\Omega$  and 100 k $\Omega$  potentiometers, .1  $\mu$ F and .22  $\mu$ F capacitors, and 1 mH and 10 mH inductors. A decade resistance box may also be useful.

Each exercise begins with an Objective and a Theory Overview. The Equipment List follows with space provided for serial numbers and measured values of components. Schematics are presented next along with the step-by-step procedure. All data tables are grouped together, typically with columns for the theoretical and experimental results, along with a column for the percent deviations between them. Finally, a group of appropriate questions are presented. For those with longer scheduled lab times, a useful addition is to simulate the circuit(s) with a SPICE-based tool such as Multisim or PSpice, and compare those results to the theoretical and experimental results as well.

A companion manual for AC electrical circuits is also available. Other manuals in this series include Semiconductor Devices (diodes, bipolar transistors and FETs), Operational Amplifiers and Linear Integrated Circuits, Computer Programming with Python™ and Multisim™, and Embedded Controllers Using C and Arduino. A text is also available for Embedded Controllers and will soon be available for Op Amps. A Semiconductor Devices text is due in 2017.

## A Note from the Author

This work was borne out of the frustration of finding a lab manual that covered all of the appropriate material at sufficient depth while remaining readable and affordable for the students. It is used at Mohawk Valley Community College in Utica, NY, for our ABET accredited AAS program in Electrical Engineering Technology. I am indebted to my students, co-workers and the MVCC family for their support and encouragement of this project. While it would have been possible to seek a traditional publisher for this work, as a long-time supporter and contributor to freeware and shareware computer software, I have decided instead to release this using a Creative Commons non-commercial, share-alike license. I encourage others to make use of this manual for their own work and to build upon it. If you do add to this effort, I would appreciate a notification.

*“Begin with the possible and move gradually towards the impossible”*

*-Robert Fripp*



# Table of Contents

1.	<a href="#">The Electrical Laboratory</a>	.	.	.	.	8
2.	<a href="#">DC Sources and Metering</a>	.	.	.	.	15
3.	<a href="#">Resistor Color Code</a>	.	.	.	.	18
4.	<a href="#">Ohm's Law</a>	.	.	.	.	24
5.	<a href="#">Series DC Circuits</a>	.	.	.	.	28
6.	<a href="#">Parallel DC Circuits</a>	.	.	.	.	32
7.	<a href="#">Series-Parallel DC Circuits</a>	.	.	.	.	36
8.	<a href="#">Ladders and Bridges</a>	.	.	.	.	40
9.	<a href="#">Potentiometers and Rheostats</a>	.	.	.	.	44
10.	<a href="#">Superposition Theorem</a>	.	.	.	.	48
11.	<a href="#">Thevenin's Theorem</a>	.	.	.	.	52
12.	<a href="#">Maximum Power Transfer</a>	.	.	.	.	56
13.	<a href="#">Mesh Analysis</a>	.	.	.	.	60
14.	<a href="#">Nodal Analysis</a>	.	.	.	.	64
15.	<a href="#">Capacitors and Inductors</a>	.	.	.	.	68
Appendix A:	<a href="#">Technical Report Guidelines</a>	.	.	.	.	72
Appendix B:	<a href="#">Example Technical Report</a>	.	.	.	.	74
Appendix C:	<a href="#">Creating Graphs Using a Spreadsheet</a>	.	.	.	.	79

# 1

## The Electrical Laboratory

### Objective

The laboratory emphasizes the practical, hands-on component of this course. It complements the theoretical material presented in lecture, and as such, is integral and indispensable to the mastery of the subject. There are several items of importance here including proper safety procedures, required tools, and laboratory reports. This exercise will finish with an examination of scientific and engineering notation, the standard form of representing and manipulating values.

### Lab Safety and Tools

If proper procedures are followed, the electrical lab is a perfectly safe place in which to work. There are some basic rules: No food or drink is allowed in lab at any time. Liquids are of particular danger as they are ordinarily conductive. While the circuitry used in lab is normally of no shock hazard, some of the test equipment may have very high internal voltages that could be lethal (in excess of 10,000 volts). Spilling a bottle of water or soda onto such equipment could leave the experimenter in the receiving end of a severe shock. Similarly, items such as books and jackets should not be left on top of the test equipment as it could cause overheating.

Each lab bench is self contained. All test equipment is arrayed along the top shelf. Beneath this shelf at the back of the work area is a power strip. All test equipment for this bench should be plugged into this strip. None of this equipment should be plugged into any other strip. This strip is controlled by a single circuit breaker which also controls the bench light. In the event of an emergency, all test equipment may be powered off through this one switch. Further, the benches are controlled by dedicated circuit breakers in the front of the lab. Next to this main power panel is an A/B/C class fire extinguisher suitable for electrical fires. Located at the rear of the lab is a safety kit. This contains bandages, cleaning swaps and the like for small cuts and the like. For serious injury, the Security Office will be contacted.

A lab bench should always be left in a secure mode. This means that the power to each piece of test equipment should be turned off, the bench itself should be turned off, all AC and DC power and signal sources should be turned down to zero, and all other equipment and components properly stowed with lab stools pushed under the bench.




It is important to come prepared to lab. This includes the class text, the lab exercise for that day, class notebook, calculator, and hand tools. The tools include an electronic breadboard, test leads, wirestrippers, and needlenose pliers or hemostats. A small pencil soldering iron may also be useful. A basic DMM (digital multimeter) rounds out the list.

A typical breadboard or protoboard is shown below:



This particular unit features two main wiring sections with a common strip section down the center. Boards can be larger or smaller than this and may or may not have the mounting plate as shown. The connections are spaced 0.1 inch apart which is the standard spacing for many semiconductor chips. These are clustered in groups of five common terminals to allow multiple connections. The exception is the common strip which may have dozens of connection points. These are called *buses* and are designed for power and ground connections. Interconnections are normally made using small diameter solid hookup wire, usually AWG 22 or 24. Larger gauges may damage the board while smaller gauges do not always make good connections and are easy to break.

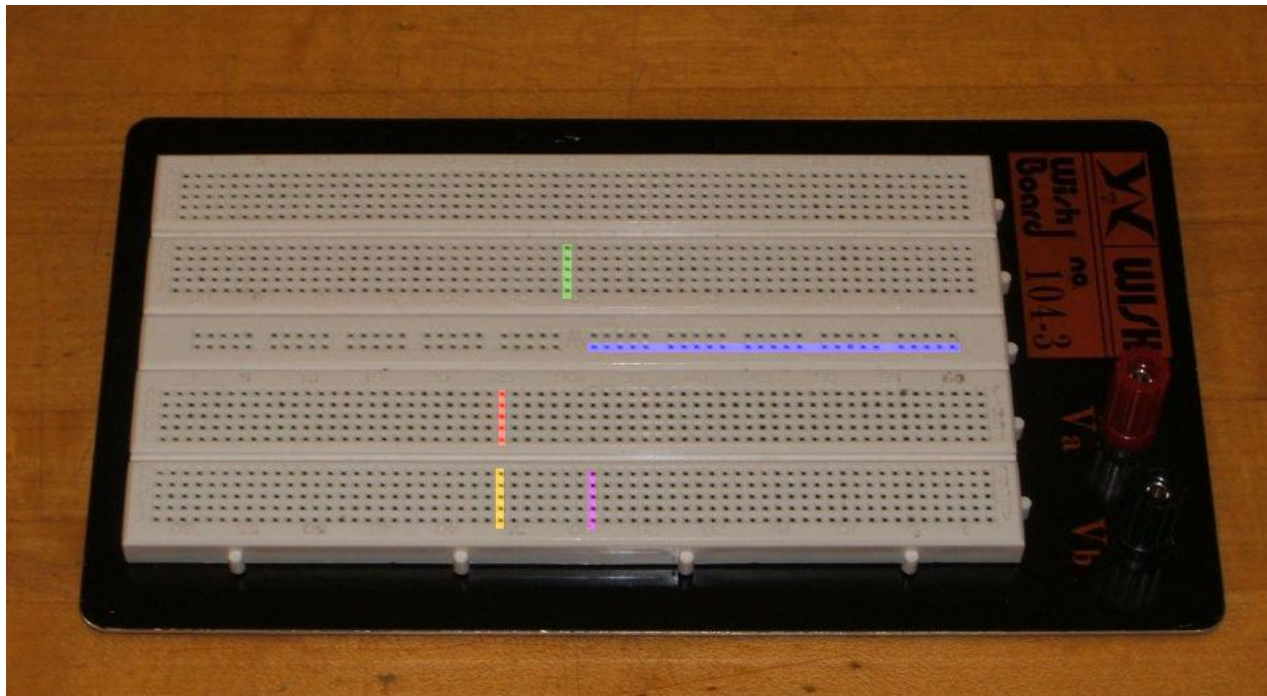In the picture below, the color highlighted sections indicate common connection points. Note the long blue section which is a bus. This unit has four discrete buses available. When building circuits on a breadboard, it is important to keep the interconnecting wires short and the layout as neat as possible. This will aid both circuit functioning and ease of troubleshooting.



## Laboratory Reports

Unless specified otherwise, all lab exercises require a non-formal laboratory report. Lab reports are individual endeavors not group work. The deadline for reports is one week after the exercise is performed. A letter grade is subtracted for the first half-week late and two letter grades are subtracted for the second half-week late. Reports are not acceptable beyond one week late. A basic report should include a statement of the Objective (i.e., those items under investigation), a Conclusion (what was found or verified), a Discussion (an explanation and analysis of the lab data which links the Objective to the Conclusion), Data Tables and Graphs, and finally, answers to any problems or questions posed in the exercise. Details of the structure of the report along with an example report may be found at <http://www2.mvcc.edu/users/faculty/jfiore/reportformat.html>

## Scientific and Engineering Notation

Scientists and engineers often work with very large and very small numbers. The ordinary practice of using commas and leading zeroes proves to be very cumbersome in this situation. Scientific notation is more compact and less error prone method of representation. The number is split into two portions: a precision part (the mantissa) and a magnitude part (the exponent, being a power of ten). For example, the value 23,000 could be written as 23 times 10 to the 3<sup>rd</sup> power (that is, times one thousand). The exponent may be thought of in terms of how places the decimal point is moved to the left. Spelling this out is awkward, so a shorthand method is used where “times 10 to the X power” is replaced by the letter E (which stands for exponent). Thus, 23,000 could be written as 23E3. The value 45,000,000,000 would be written as 45E9. Note that it would also be possible to write this number as 4.5E10 or even .45E11. The

only difference between scientific notation and engineering notation is that for engineering notation the exponent is always a multiple of three. Thus, 45E9 is proper engineering notation but 4.5E10 isn't. On most scientific calculators E is represented by either an "EE" or "EXP" button. The process of entering the value 45E9 would be depressing the keys 4 5 EE 9.

For fractional values, the exponent is negative and may be thought of in terms how many places the decimal point must be moved to the right. Thus, .00067 may be written as .67E-3 or 6.7E-4 or even 670E-6. Note that only the first and last of these three are acceptable as engineering notation.

Engineering notation goes one step further by using a set of prefixes to replace the multiples of three for the exponent. The prefixes are:

E12 = Tera (T)	E9 = Giga (G)	E6 = Mega (M)	E3 = kilo (k)
E-3 = milli (m)	E-6 = micro ( $\mu$ )	E-9 = nano (n)	E-12 = pico (p)

Thus, 23,000 volts could be written as 23E3 volts or simply 23 kilovolts.

Besides being more compact, this notation is much simpler than the ordinary form when manipulating wide ranging values. When multiplying, simply multiply the precision portions and add the exponents. Similarly, when dividing, divide the precision portions and subtract the exponents. For example, 23,000 times .000003 may appear to be a complicated task. In engineering notation this is 23E3 times 3E-6. The result is 69E-3 (that is, .069). Given enough practice it will become second nature that kilo (E3) times micro (E-6) yields milli (E-3). This will facilitate lab estimates a great deal. Continuing, 42,000,000 divided by .002 is 42E6 divided by 2E-3, or 21E9 (the exponent is 6 minus a negative 3, or 9).

When adding or subtracting, first make sure that the exponents are the same (scaling if required) and then add or subtract the precision portions. For example, 2E3 plus 5E3 is 7E3. By comparison, 2E3 plus 5E6 is the same as 2E3 plus 5000E3, or 5002E3 (or 5.002E6).

Perform the following operations. Convert the following into scientific and engineering notation.

- |          |               |
|----------|---------------|
| 1. 1,500 | 2. 63,200,000 |
| 3. .0234 | 4. .000059    |
| 5. 170   |               |

Convert the following into normal longhand notation:

- |            |           |
|------------|-----------|
| 6. 1.23E3  | 7. 54.7E6 |
| 8. 2E-3    | 9. 27E-9  |
| 10. 4.39E7 |           |

Use the appropriate prefix for the following:

11. 4E6 volts

12. 5.1E3 feet

13. 3.3E-6 grams

Perform the following operations:

14.  $5.2\text{E}6 + 1.7\text{E}6$

15.  $12\text{E}3 - 900$

16.  $1.7\text{E}3 \cdot 2\text{E}6$

17.  $48\text{E}3 / 4\text{E}6$

18.  $20 / 4\text{E}3$

19.  $10\text{ M} \cdot 2\text{ k}$

20.  $8\text{ n} / 2\text{ m}$



# 2

## DC Sources and Metering

### Objective

The objective of this exercise is to become familiar with the operation and usage of basic DC electrical laboratory devices, namely DC power supplies and digital multimeters.

### Theory Overview

The adjustable DC power supply is a mainstay of the electrical and electronics laboratory. It is indispensable in the prototyping of electronic circuits and extremely useful when examining the operation of DC systems. Of equal importance is the handheld digital multimeter or DMM. This device is designed to measure voltage, current, and resistance at a minimum, although some units may offer the ability to measure other parameters such as capacitance or transistor beta. Along with general familiarity of the operation of these devices, it is very important to keep in mind that no measurement device is perfect; their relative *accuracy*, *precision*, and *resolution* must be taken into account. *Accuracy* refers to how far a measurement is from that parameter's true value. *Precision* refers to the repeatability of the measurement, that is, the sort of variance (if any) that occurs when a parameter is measured several times. For a measurement to be valid, it must be both accurate and repeatable. Related to these characteristics is *resolution*. Resolution refers to the smallest change in measurement that may be discerned. For digital measurement devices this is ultimately limited by the number of significant digits available to display.

A typical DMM offers 3 ½ digits of resolution, the half-digit referring to a leading digit that is limited to zero or one. This is also known as a “2000 count display”, meaning that it can show a minimum of 0000 and a maximum of 1999. The decimal point is “floating” in that it could appear anywhere in the sequence. Thus, these 2000 counts could range from 0.000 volts up to 1.999 volts, or 00.00 volts to 19.99 volts, or 000.0 volts to 199.9 volts, and so forth. With this sort of limitation in mind, it is very important to set the DMM to the lowest range that won't produce an overload in order to achieve the greatest accuracy.

A typical accuracy specification would be 1% of full scale plus two counts. “Full scale” refers to the selected range. If the 2 volt range was selected (0.000 to 1.999 for a 3 ½ digit meter), 1% would be approximately 20 millivolts (0.02 volts). To this a further uncertainty of two counts (i.e., the finest digit) must be included. In this example, the finest digit is a millivolt (0.001 volts) so this adds another 2 millivolts for a total of 22 millivolts of potential inaccuracy. In other words, the value displayed by the meter could be as much as 22 millivolts higher or lower than the true value. For the 20 volt range the inaccuracy would be computed in like manner for a total of 220 millivolts. Obviously, if a signal in the vicinity of, say, 1.3 volts was to be measured, greater accuracy will be obtained on the 2 volt scale than on either the 20 or 200 volt scales. In contrast, the 200 millivolt scale would produce an overload situation and cannot be used. Overloads are often indicated by either a flashing display or a readout of “OL”.

## Equipment

- (1) Adjustable DC Power Supply      model: \_\_\_\_\_ srn: \_\_\_\_\_  
(1) Digital Multimeter              model: \_\_\_\_\_ srn: \_\_\_\_\_  
(1) Precision Digital Multimeter      model: \_\_\_\_\_ srn: \_\_\_\_\_

## Procedure

1. Assume a general purpose 3  $\frac{1}{2}$  digit DMM is being used. Its base accuracy is listed as 2% of full scale plus 5 counts. Compute the inaccuracy caused by the scale and count factors and determine the total. Record these values in Table 2.1.
2. Repeat step one for a precision 4  $\frac{1}{2}$  digit DMM spec'd at .5% full scale plus 3 counts. Record results in Table 2.2.
3. Set the adjustable power supply to 2.2 volts via its display. Use both the Coarse and Fine controls to get as close to 2.2 volts as possible. Record the displayed voltage in the first column of Table 2.3. Using the general purpose DMM set to the DC voltage function, set the range to 20 volts full scale. Measure the voltage at the output jacks of the power supply. Be sure to connect the DMM and power supply red lead to red lead, and black lead to black lead. Record the voltage registered by the DMM in the middle column of Table 2.3. Reset the DMM to the 200 volt scale, re-measure the voltage, and record in the final column.
4. Repeat step three for the remaining voltages of Table 2.3.
5. Using the precision DMM, repeat steps three and four, recording the results in Table 2.4.

## Data Tables

Scale	2% FS	5 Counts	Total
200 mV			
20 V			

Table 2.1

Scale	.5% FS	3 Counts	Total
200 mV			
2 V			

Table 2.2

Voltage	Power Supply	DMM 20V Scale	DMM 200V Scale
2.2			
5.0			
9.65			
15.0			

Table 2.3

Voltage	Power Supply	DMM 20V Scale	DMM 200V Scale
2.2			
5.0			
9.65			
15.0			

Table 2.4

## Questions

1. For the general purpose DMM of Table 2.1, which contributes the larger share of inaccuracy; the full scale percentage or the count spec?
2. Bearing in mind that the power supply display is really just a very limited sort of digital volt meter, which voltages in Table 2.3 and 2.4 do you suspect to be the most accurately measured and why?
3. Assuming that the precision DMM used in Table 2.4 has a base accuracy spec of .1% plus 2 counts and is properly calibrated, what is the range of possible “true” voltages measured for 15.0 volts on the 20 volt scale?





# 3

## Resistor Color Code


### Objective

The objective of this exercise is to become familiar with the measurement of resistance values using a digital multimeter (DMM). A second objective is to learn the resistor color code.
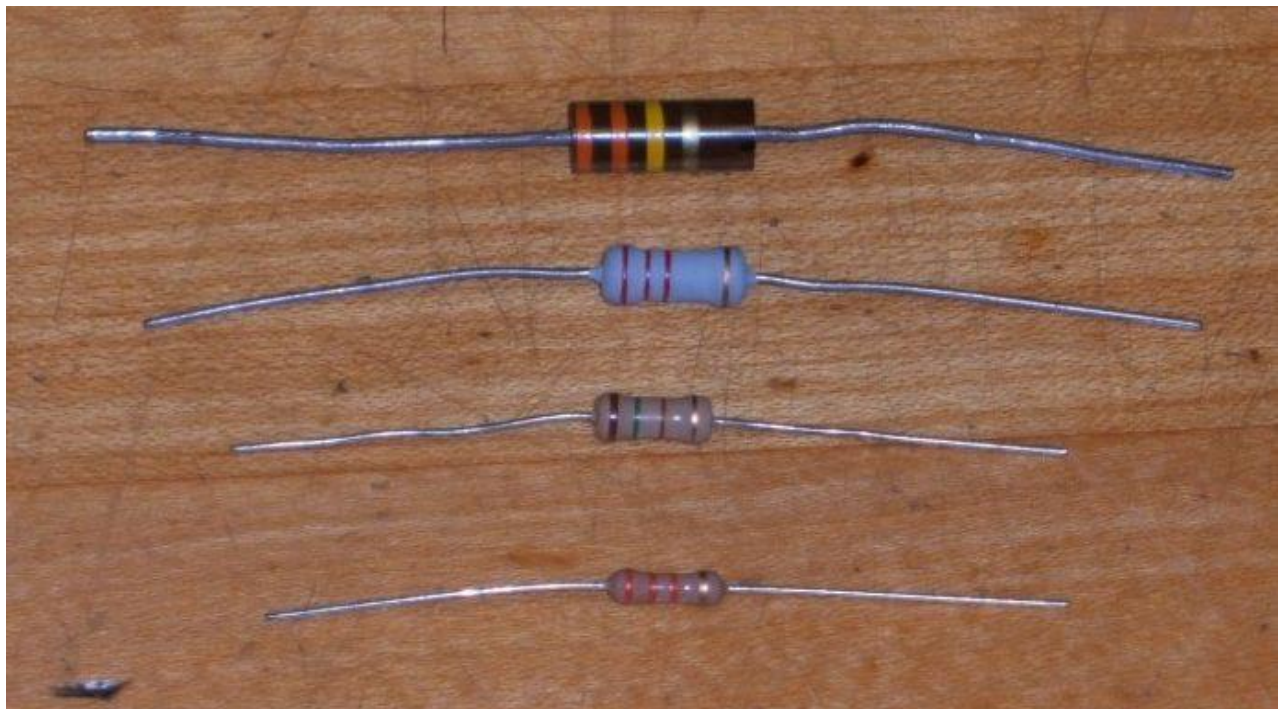
### Theory Overview

The resistor is perhaps the most fundamental of all electrical devices. Its fundamental attribute is the restriction of electrical current flow: The greater the resistance, the greater the restriction of current. Resistance is measured in Ohms. The measurement of resistance in unpowered circuits may be performed with a digital multimeter. Like all components, resistors cannot be manufactured to perfection. That is, there will always be some variance of the true value of the component when compared to its nameplate or nominal value. For precision resistors, typically 1% tolerance or better, the nominal value is usually printed directly on the component. Normally, general purpose components, i.e. those worse than 1%, usually use a color code to indicate their value.

The resistor color code typically uses 4 color bands. The first two bands indicate the precision values (i.e. the mantissa) while the third band indicates the power of ten applied (i.e. the number of zeroes to add). The fourth band indicates the tolerance. It is possible to find resistors with five or six bands but they will not be examined in this exercise. Examples are shown below:



It is important to note that the physical size of the resistor indicates its power dissipation rating, not its ohmic value.

Each color in the code represents a numeral. It starts with black and finishes with white, going through the rainbow in between:

0 Black	1 Brown	2 Red	3 Orange	4 Yellow
5 Green	6 Blue	7 Violet	8 Gray	9 White

For the fourth, or tolerance, band:

5% Gold	10% Silver	20% None
---------	------------	----------

For example, a resistor with the color code brown-red-orange-silver would correspond to 1 2 followed by 3 zeroes, or 12,000 Ohms (more conveniently, 12 k Ohms). It would have a tolerance of 10% of 12 k Ohms or 1200 Ohms. This means that the actual value of any particular resistor with this code could be anywhere between  $12,000 - 1200 = 10,800$ , to  $12,000 + 1200 = 13,200$ . That is, 10.8 k to 13.2 k Ohms. Note, the IEC standard replaces the decimal point with the engineering prefix, thus 1.2 k is alternately written 1k2.

Similarly, a 470 k 5% resistor would have the color code yellow-violet-yellow-gold. To help remember the color code many mnemonics have been created using the first letter of the colors to create a sentence. One example is the *picnic mnemonic* **Black Bears Robbed Our Yummy Goodies Beating Various Gray Wolves**.

Measurement of resistors with a DMM is a very straight forward process. Simply set the DMM to the resistance function and choose the first scale that is higher than the expected value. Clip the leads to the resistor and record the resulting value.

## Equipment

(1) Digital Multimeter                      model: \_\_\_\_\_ srn: \_\_\_\_\_

## Procedure

1. Given the nominal values and tolerances in Table 3.1, determine and record the corresponding color code bands.
2. Given the color codes in Table 3.2, determine and record the nominal value, tolerance and the minimum and maximum acceptable values.
3. Obtain a resistor equal to the first value listed in Table 3.3. Determine the minimum and maximum acceptable values based on the nominal value and tolerance. Record these values in Table 3.3. Using the DMM, measured the actual value of the resistor and record it in Table 3.3. Determine the deviation percentage of this component and record it in Table 3.3. The deviation percentage may be found via:  $\text{Deviation} = 100 * (\text{measured-nominal})/\text{nominal}$ . *Circle the deviation if the resistor is out of tolerance.*
4. Repeat Step 3 for the remaining resistor in Table 3.3.

## Data Tables

Value	Band 1	Band 2	Band 3	Band 4
27 @ 10%				
56 @ 10%				
180 @ 5%				
390 @ 10%				
680 @ 5%				
1.5 k @ 20%				
3.6 k @ 10%				
7.5 k @ 5%				
10 k @ 5%				
47 k @ 10%				
820 k @ 10%				
2.2 M @ 20 %				

Table 3.1

Colors	Nominal	Tolerance	Minimum	Maximum
red-red-black-silver				
blue-gray-black-gold				
brown-green-brown-gold				
orange-orange-brown-silver				
green-blue-brown –gold				
brown-red-red–silver				
red-violet-red–silver				
gray-red-red–gold				
brown-black-orange–gold				
orange-orange-orange–silver				
blue-gray-yellow–none				
green-black-green-silver				

Table 3.2

Value	Minimum	Maximum	Measured	Deviation
22 @ 10%				
68 @ 5%				
150 @ 5%				
330 @ 10%				
560 @ 5%				
1.2 k @ 5%				
2.7 k @ 10%				
8.2 k @ 5%				
10 k @ 5%				
33 k @ 10%				
680 k @ 10%				
5 M @ 20 %				

Table 3.3

## Questions

1. What is the largest deviation in Table 3.3? Would it ever be possible to find a value that is outside the stated tolerance? Why or why not?
2. If Steps 3 and 4 were to be repeated with another batch of resistors, would the final two columns be identical to the original Table 3.3? Why or why not?
3. Do the measured values of Table 3.3 represent the exact values of the resistors tested? Why or why not?



# 4

## Ohm's Law

### Objective

This exercise examines Ohm's law, one of the fundamental laws governing electrical circuits. It states that voltage is equal to the product of current times resistance.

### Theory Overview

Ohm's law is commonly written as  $V = I * R$ . That is, for a given current, an increase in resistance will result in a greater voltage. Alternately, for a given voltage, an increase in resistance will produce a decrease in current. As this is a first order linear equation, plotting current versus voltage for a fixed resistance will yield a straight line. The slope of this line is the conductance, and conductance is the reciprocal of resistance. Therefore, for a high resistance, the plot line will appear closer to the horizontal while a lower resistance will produce a more vertical plot line.

### Equipment

- |                                |             |           |
|--------------------------------|-------------|-----------|
| (1) Adjustable DC Power Supply | model:_____ | srn:_____ |
| (1) Digital Multimeter         | model:_____ | srn:_____ |
| (1) 1 k $\Omega$ resistor      | _____       |           |
| (1) 6.8 k $\Omega$ resistor    | _____       |           |
| (1) 33 k $\Omega$ resistor     | _____       |           |

### Schematic

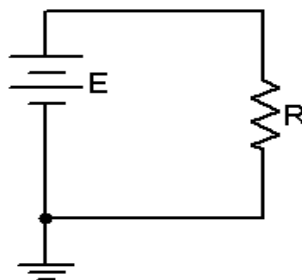


Figure 4.1



## Procedure

1. Build the circuit of Figure 4.1 using the 1 k $\Omega$  resistor. Set the DMM to measure DC current and insert it in-line between the source and resistor. Set the source for zero volts. Measure and record the current in Table 4.1. Note that the theoretical current is 0 and any measured value other than 0 would produce an undefined percent deviation.
2. Setting E at 2 volts, determine the theoretical current based on Ohm's law and record this in Table 4.1. Measure the actual current, determine the deviation, and record these in Table 4.1. Note that  $\text{Deviation} = 100 * (\text{measured} - \text{theory}) / \text{theory}$ .
3. Repeat step 2 for the remaining source voltages in Table 4.1.
4. Remove the 1 k $\Omega$  and replace it with the 6.8 k $\Omega$ . Repeat steps 1 through 3 using Table 4.2.
5. Remove the 6.8 k $\Omega$  and replace it with the 33 k $\Omega$ . Repeat steps 1 through 3 using Table 4.3.
6. Using the measured currents from Tables 4.1, 4.2, and 4.3, create a plot of current versus voltage. Plot all three curves on the same graph. Voltage is the horizontal axis and current is the vertical axis.

## Data Tables

E (volts)	I theory	I measured	Deviation
0	0		
2			
4			
6			
8			
10			
12			

Table 4.1 (1 k $\Omega$ )

E (volts)	I theory	I measured	Deviation
0	0		
2			
4			
6			
8			
10			
12			

Table 4.2 (6.8 k $\Omega$ )

E (volts)	I theory	I measured	Deviation
0	0		
2			
4			
6			
8			
10			
12			

Table 4.3 (33 k $\Omega$ )

## Questions

1. Does Ohm's Law appear to hold in this exercise?
2. Is there a linear relationship between current and voltage?
3. What is the relationship between the slope of the plot line and the circuit resistance?



# 5

## Series DC Circuits

### Objective

The focus of this exercise is an examination of basic series DC circuits with resistors. A key element is Kirchhoff's Voltage Law which states that the sum of voltage rises around a loop must equal the sum of the voltage drops. The voltage divider rule will also be investigated.

### Theory Overview

A series circuit is defined by a single loop in which all components are arranged in daisy-chain fashion. The current is the same at all points in the loop and may be found by dividing the total voltage source by the total resistance. The voltage drops across any resistor may then be found by multiplying that current by the resistor value. Consequently, the voltage drops in a series circuit are directly proportional to the resistance. An alternate technique to find the voltage is the voltage divider rule. This states that the voltage across any resistor (or combination of resistors) is equal to the total voltage source times the ratio of the resistance of interest to the total resistance.

### Equipment

- |                                |                        |
|--------------------------------|------------------------|
| (1) Adjustable DC Power Supply | model: _____ sm: _____ |
| (1) Digital Multimeter         | model: _____ sm: _____ |
| (1) 1 k $\Omega$               | _____                  |
| (1) 2.2 k $\Omega$             | _____                  |
| (1) 3.3 k $\Omega$             | _____                  |
| (1) 6.8 k $\Omega$             | _____                  |

### Schematics

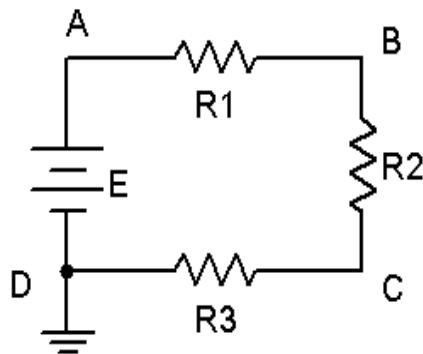


Figure 5.1

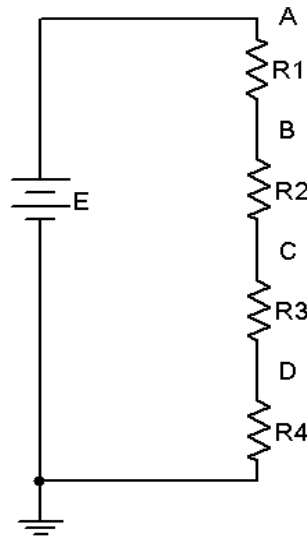


Figure 5.2

## Procedure

1. Using the circuit of Figure 5.1 with  $R_1 = 1\text{ k}$ ,  $R_2 = 2.2\text{ k}$ ,  $R_3 = 3.3\text{ k}$ , and  $E = 10\text{ volts}$ , determine the theoretical current and record it in Table 5.1. Construct the circuit. Set the DMM to read DC current and insert it in the circuit at point A. Remember, ammeters go in-line and require the circuit to be opened for proper measurement. The red lead should be placed closer to the positive source terminal. Record this current in Table 5.1. Repeat the current measurements at points B and C.
2. Using the theoretical current found in Step 1, apply Ohm's law to determine the expected voltage drops across  $R_1$ ,  $R_2$ , and  $R_3$ . Record these values in the Theory column of Table 5.2.
3. Set the DMM to measure DC voltage. Remember, unlike current, voltage is measured across components. Place the DMM probes across  $R_1$  and measure its voltage. Again, red lead should be placed closer to the positive source terminal. Record this value in Table 5.2. Repeat this process for the voltages across  $R_2$  and  $R_3$ . Determine the percent deviation between theoretical and measured for each of the three resistor voltages and record these in the final column of Table 5.2.
4. Consider the circuit of Figure 5.2 with  $R_1 = 1\text{ k}$ ,  $R_2 = 2.2\text{ k}$ ,  $R_3 = 3.3\text{ k}$ ,  $R_4 = 6.8\text{ k}$  and  $E = 20\text{ volts}$ . Using the voltage divider rule, determine the voltage drops across each of the four resistors and record the values in Table 5.3 under the Theory column. Note that the larger the resistor, the greater the voltage should be. Also determine the potentials  $V_{AC}$  and  $V_B$ , again using the voltage divider rule.
5. Construct the circuit of Figure 5.2 with  $R_1 = 1\text{ k}$ ,  $R_2 = 2.2\text{ k}$ ,  $R_3 = 3.3\text{ k}$ ,  $R_4 = 6.8\text{ k}$  and  $E = 20\text{ volts}$ . Set the DMM to measure DC voltage. Place the DMM probes across  $R_1$  and measure its voltage. Record this value in Table 5.3. Also determine the deviation. Repeat this process for the remaining three resistors.

6. To find  $V_{AC}$ , place the red probe on point A and the black probe on point C. Similarly, to find  $V_B$ , place the red probe on point B and the black probe on ground. Record these values in Table 5.3 with deviations.

## Data Tables

I Theory	I Point A	I Point B	I Point C

Table 5.1

Voltage	Theory	Measured	Deviation
R1			
R2			
R3			

Table 5.2

Voltage	Theory	Measured	Deviation
R1			
R2			
R3			
R4			
$V_{AC}$			
$V_B$			

Table 5.3

## Questions

1. For the circuit of Figure 5.1, what is the expected current measurement at point D?
2. For the circuit of Figure 5.2, what are the expected current and voltage measurements at point D?
3. In Figure 5.2,  $R_4$  is approximately twice the size of  $R_3$  and about three times the size of  $R_2$ . Would the voltages exhibit the same ratios? Why/why not? What about the currents through the resistors?
4. If a fifth resistor of  $10\text{ k}\Omega$  was added below  $R_4$  in Figure 5.2, how would this alter  $V_{AC}$  and  $V_B$ ? Show work.
5. Is KVL satisfied in Tables 5.2 and 5.3?

# 6

## Parallel DC Circuits

### Objective

The focus of this exercise is an examination of basic parallel DC circuits with resistors. A key element is Kirchhoff's Current Law which states that the sum of currents entering a node must equal the sum of the currents exiting that node. The current divider rule will also be investigated.

### Theory Overview

A parallel circuit is defined by the fact that all components share two common nodes. The voltage is the same across all components and will equal the applied source voltage. The total supplied current may be found by dividing the voltage source by the equivalent parallel resistance. It may also be found by summing the currents in all of the branches. The current through any resistor branch may be found by dividing the source voltage by the resistor value. Consequently, the currents in a parallel circuit are inversely proportional to the associated resistances. An alternate technique to find a particular current is the current divider rule. For a two resistor circuit this states that the current through one resistor is equal to the total current times the ratio of the other resistor to the total resistance.

### Equipment

- |                                |                       |
|--------------------------------|-----------------------|
| (1) Adjustable DC Power Supply | model:_____ srn:_____ |
| (1) Digital Multimeter         | model:_____ srn:_____ |
| (1) 1 k $\Omega$               | _____                 |
| (1) 2.2 k $\Omega$             | _____                 |
| (1) 3.3 k $\Omega$             | _____                 |
| (1) 6.8 k $\Omega$             | _____                 |

### Schematics

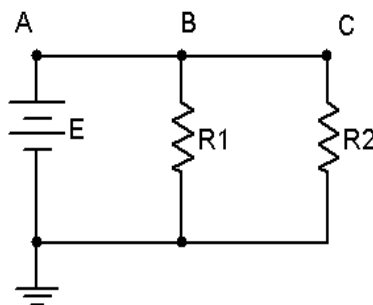


Figure 6.1



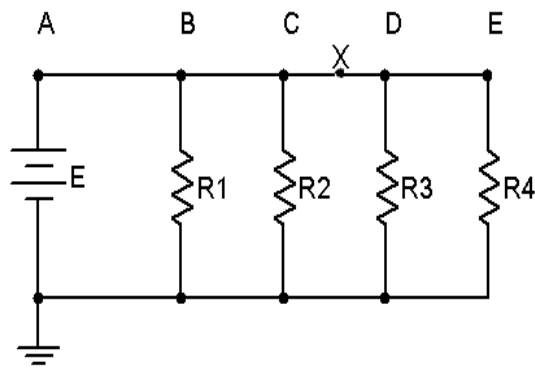


Figure 6.2

## Procedure

1. Using the circuit of Figure 6.1 with  $R1 = 1\text{ k}$ ,  $R2 = 2.2\text{ k}$  and  $E = 8\text{ volts}$ , determine the theoretical voltages at points A, B, and C with respect to ground. Record these values in Table 6.1. Construct the circuit. Set the DMM to read DC voltage and apply it to the circuit from point A to ground. The red lead should be placed at point A and the black lead should be connected to ground. Record this voltage in Table 6.1. Repeat the measurements at points B and C.
2. Apply Ohm's law to determine the expected currents through  $R1$  and  $R2$ . Record these values in the Theory column of Table 6.2. Also determine and record the total current.
3. Set the DMM to measure DC current. Remember, current is measured at a single point and requires the meter to be inserted in-line. To measure the total supplied current place the DMM between points A and B. The red lead should be placed closer to the positive source terminal. Record this value in Table 6.2. Repeat this process for the currents through  $R1$  and  $R2$ . Determine the percent deviation between theoretical and measured for each of the currents and record these in the final column of Table 6.2.
4. Crosscheck the theoretical results by computing the two resistor currents through the current divider rule. Record these in Table 6.3.
5. Consider the circuit of Figure 6.2 with  $R1 = 1\text{ k}$ ,  $R2 = 2.2\text{ k}$ ,  $R3 = 3.3\text{ k}$ ,  $R4 = 6.8\text{ k}$  and  $E = 10\text{ volts}$ . Using the Ohm's law, determine the currents through each of the four resistors and record the values in Table 6.4 under the Theory column. Note that the larger the resistor, the smaller the current should be. Also determine and record the total supplied current and the current  $I_x$ . Note that this current should equal the sum of the currents through  $R3$  and  $R4$ .
6. Construct the circuit of Figure 6.2 with  $R1 = 1\text{ k}$ ,  $R2 = 2.2\text{ k}$ ,  $R3 = 3.3\text{ k}$ ,  $R4 = 6.8\text{ k}$  and  $E = 10\text{ volts}$ . Set the DMM to measure DC current. Place the DMM probes in-line with  $R1$  and measure its current. Record this value in Table 6.4. Also determine the deviation. Repeat this process for the remaining three resistors. Also measure the total current supplied by the source by inserting the ammeter between points A and B.

7. To find  $I_x$ , insert the ammeter at point X with the black probe closer to R3. Record this value in Table 6.4 with deviation.

## Data Tables

Voltage	Theory	Measured
$V_A$		
$V_B$		
$V_C$		

Table 6.1

Current	Theory	Measured	Deviation
R1			
R2			
Total			

Table 6.2

Current	CDR Theory
R1	
R2	
Total	

Table 6.3

Current	Theory	Measured	Deviation
R1			
R2			
R3			
R4			
Total			
$I_x$			

Table 6.4

## Questions

1. For the circuit of Figure 6.1, what is the expected current entering the negative terminal of the source?
2. For the circuit of Figure 6.2, what is the expected current between points B and C?
3. In Figure 6.2, R4 is approximately twice the size of R3 and about three times the size of R2. Would the currents exhibit the same ratios? Why/why not?
4. If a fifth resistor of 10 k $\Omega$  was added to the right of R4 in Figure 6.2, how would this alter  $I_{\text{Total}}$  and  $I_x$ ? Show work.
5. Is KCL satisfied in Tables 6.2 and 6.4?

# 7

## Series-Parallel DC Circuits

### Objective

This exercise will involve the analysis of basic series-parallel DC circuits with resistors. The use of simple series-only and parallel-only sub-circuits is examined as one technique to solve for desired currents and voltages.

### Theory Overview

Simple series-parallel networks may be viewed as interconnected series and parallel sub-networks. Each of these sub-networks may be analyzed through basic series and parallel techniques such as the application of voltage divider and current divider rules along with Kirchhoff's Voltage and Current Laws. It is important to identify the most simple series and parallel connections in order to jump to more complex interconnections.

### Equipment

- |                                |              |            |
|--------------------------------|--------------|------------|
| (1) Adjustable DC Power Supply | model: _____ | srn: _____ |
| (1) Digital Multimeter         | model: _____ | srn: _____ |
| (1) 1 k $\Omega$               | _____        |            |
| (1) 2.2 k $\Omega$             | _____        |            |
| (1) 4.7 k $\Omega$             | _____        |            |
| (1) 6.8 k $\Omega$             | _____        |            |

### Schematics

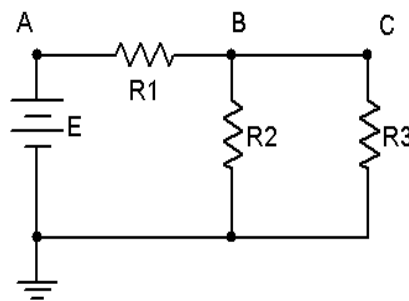


Figure 7.1

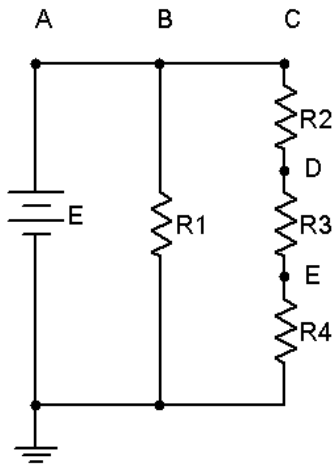


Figure 7.2

## Procedure

1. Consider the circuit of Figure 7.1 with  $R1 = 1\text{ k}$ ,  $R2 = 2.2\text{ k}$ ,  $R3 = 4.7\text{ k}$  and  $E = 10\text{ volts}$ .  $R2$  is in parallel with  $R3$ . This combination is in series with  $R1$ . Therefore, the  $R2$ ,  $R3$  pair may be treated as a single resistance to form a series loop with  $R1$ . Based on this observation, determine the theoretical voltages at points A, B, and C with respect to ground. Record these values in Table 7.1. Construct the circuit. Set the DMM to read DC voltage and apply it to the circuit from point A to ground. Record this voltage in Table 7.1. Repeat the measurements at points B and C, determine the deviations, and record the values in Table 7.1.
2. Applying KCL to the parallel sub-network, the current entering node B (i.e., the current through  $R1$ ) should equal the sum of the currents flowing through  $R2$  and  $R3$ . These currents may be determined through Ohm's Law and/or the Current Divider Rule. Compute these currents and record them in Table 7.2. Using the DMM as an ammeter, measure these three currents and record the values along with deviations in Table 7.2.
3. Consider the circuit of Figure 7.2.  $R2$ ,  $R3$  and  $R4$  create a series sub-network. This sub-network is in parallel with  $R1$ . By observation then, the voltages at nodes A, B and C should be identical as in any parallel circuit of similar construction. Due to the series connection, the same current flows through  $R2$ ,  $R3$  and  $R4$ . Further, the voltages across  $R2$ ,  $R3$  and  $R4$  should sum up to the voltage at node C, as in any similarly constructed series network. Finally, via KCL, the current exiting the source must equal the sum of the currents entering  $R1$  and  $R2$ .
4. Build the circuit of Figure 7.2 with  $R1 = 1\text{ k}$ ,  $R2 = 2.2\text{ k}$ ,  $R3 = 4.7\text{ k}$ ,  $R4 = 6.8\text{ k}$  and  $E = 20\text{ volts}$ . Using the series and parallel relations noted in Step 3, calculate the voltages at points B, C, D and E. Measure these potentials with the DMM, determine the deviations, and record the values in Table 7.3.

- Calculate the currents leaving the source and flowing through R1 and R2. Record these values in Table 7.4. Using the DMM as an ammeter, measure those same currents, compute the deviations, and record the results in Table 7.4.

## Multisim

- Build the circuit of Figure 7.1 in Multisim. Using the virtual DMM as a voltmeter determine the voltages at nodes A, B and C, and compare these to the theoretical and measured values recorded in Table 7.1.
- Build the circuit of Figure 7.2 in Multisim. Using the DC Operating Point simulation function, determine the voltages at nodes B, C, D and E, and compare these to the theoretical and measured values recorded in Table 7.3.

## Data Tables

Voltage	Theory	Measured	Deviation
$V_A$			
$V_B$			
$V_C$			

Table 7.1

Current	Theory	Measured	Deviation
$R_1$			
$R_2$			
$R_3$			

Table 7.2

Voltage	Theory	Measured	Deviation
$V_B$			
$V_C$			
$V_D$			
$V_E$			

Table 7.3

Current	Theory	Measured	Deviation
Source			
R1			
R2			

Table 7.4

## Questions

1. Are KVL and KCL satisfied in Tables 7.1 and 7.2?
2. Are KVL and KCL satisfied in Tables 7.3 and 7.4?
3. How would the voltages at A and B in Figure 7.1 change if a fourth resistor equal to 10 k was added in parallel with R3? What if this resistor was added in series with R3?
4. How would the currents through R1 and R2 in Figure 7.2 change if a fifth resistor equal to 10 k was added in series with R1? What if this resistor was added in parallel with R1?

# 8

## Ladders and Bridges

### Objective

The objective of this exercise is to continue the exploration of basic series-parallel DC circuits. The basic ladder network and bridge are examined. A key element here is the concept of loading, that is, the effect that a sub-circuit may have on a neighboring sub-circuit.

### Theory Overview

Ladder networks are comprised of a series of alternating series and parallel connections. Each section effectively loads the prior section, meaning that the voltage and current of the prior section may change considerably if the loading section is removed. One possible technique for the solution of ladder networks is a series of cascading voltage dividers. Current dividers may also be used. In contrast, bridge networks typically make use of four elements arranged in dual series and parallel configuration. These are often used in measurement systems with the voltage of interest derived from the difference of two series sub-circuit voltages. As in the simpler series-parallel networks; KVL, KCL, the current divider rule and the voltage divider rule may be used in combination to analyze the sub-circuits.

### Equipment

(1) Adjustable DC Power Supply	model:_____	sn:_____
(1) Digital Multimeter	model:_____	sn:_____
(1) 1 k $\Omega$	_____	
(1) 2.2 k $\Omega$	_____	
(1) 3.3 k $\Omega$	_____	
(1) 6.8 k $\Omega$	_____	
(1) 10 k $\Omega$	_____	
(1) 22 k $\Omega$	_____	



## Schematics

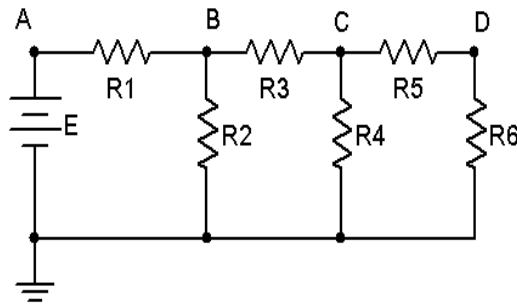


Figure 8.1

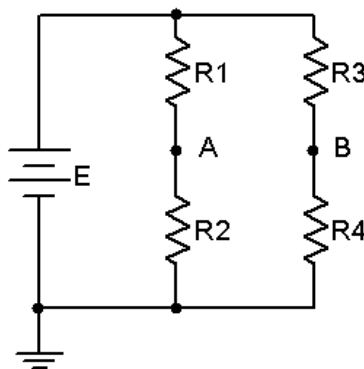


Figure 8.2

## Procedure

1. Consider the circuit of Figure 8.1. R5 and R6 form a simple series connection. Together, they are in parallel with R4. Therefore the voltage across R4 must be the same as the sum of the voltages across R5 and R6. Similarly, the current entering node C from R3 must equal the sum of the currents flowing through R4 and R5. This three resistor combination is in series with R3 in much the same manner than R6 is in series with R5. These four resistors are in parallel with R2, and finally, these five resistors are in series with R1. Note that to find the voltage at node B the voltage divider rule may be used, *however*, it is important to note that VDR cannot be used in terms of R1 versus R2. Instead, R1 reacts against the entire series-parallel combination of R2 through R6. Similarly, R3 reacts against the combination of R4, R5 and R6. That is to say R5 and R6 *load* R4, and R3 through R6 *load* R2. Because of this process note that  $V_D$  must be less than  $V_C$ , which must be less than  $V_B$ , which must be less than  $V_A$ . Thus the circuit may be viewed as a sequence of loaded voltage dividers.
2. Construct the circuit of Figure 8.1 using  $R1 = 1\text{ k}$ ,  $R2 = 2.2\text{ k}$ ,  $R3 = 3.3\text{ k}$ ,  $R4 = 6.8\text{ k}$ ,  $R5 = 10\text{ k}$ ,  $R6 = 22\text{ k}$ , and  $E = 20\text{ volts}$ . Based on the observations of Step 1, determine the theoretical voltages at nodes A, B, C and D, and record them in Table 8.1. Measure the potentials with a DMM, compute the deviations and record the results in Table 8.1.

3. Based on the theoretical voltages found in Table 8.1, determine the currents through R1, R2, R4 and R6. Record these values in Table 8.2. Measure the currents with a DMM, compute the deviations and record the results in Table 8.2.
4. Consider the circuit of Figure 8.2. In this bridge network, the voltage of interest is  $V_{AB}$ . This may be directly computed from  $V_A - V_B$ . Assemble the circuit using  $R_1 = 1\text{ k}$ ,  $R_2 = 2.2\text{ k}$ ,  $R_3 = 10\text{ k}$ ,  $R_4 = 6.8\text{ k}$  and  $E = 10\text{ volts}$ . Determine the theoretical values for  $V_A$ ,  $V_B$  and  $V_{AB}$  and record them in Table 8.3. Note that the voltage divider rule is very effective here as the  $R_1\ R_2$  branch and the  $R_3\ R_4$  branch are in parallel and therefore both “see” the source voltage.
5. Use the DMM to measure the potentials at A and B with respect to ground, the red lead going to the point of interest and the black lead going to ground. To measure the voltage from A to B, the red lead is connected to point A while the black is connected to point B. Record these potentials in Table 8.3. Determine the deviations and record these in Table 8.3.

## Data Tables

Voltage	Theory	Measured	Deviation
$V_A$			
$V_B$			
$V_C$			
$V_D$			

Table 8.1

Current	Theory	Measured	Deviation
$R_1$			
$R_2$			
$R_4$			
$R_6$			

Table 8.2

Voltage	Theory	Measured	Deviation
$V_A$			
$V_B$			
$V_{AB}$			

Table 8.3

## Questions

1. In Figure 8.1, if another pair of resistors was added across  $R_6$ , would  $V_D$  go up, down, or stay the same? Why?
2. In Figure 8.1, if  $R_4$  was accidentally opened would this change the potentials at B, C and D? Why or why not?
3. If the DMM leads are reversed in Step 5, what happens to the measurements in Table 8.3?
4. Suppose that  $R_3$  and  $R_4$  are accidentally swapped in Figure 8.2. What is the new  $V_{AB}$ ?

# 9

## Potentiometers and Rheostats

### Objective

The objective of this exercise is to examine the practical workings of adjustable resistances, namely the potentiometer and rheostat. Their usage in adjustable voltage and current control will be investigated.

### Theory Overview

A potentiometer is a three terminal resistive device. The outer terminals present a constant resistance which is the nominal value of the device. A third terminal, called the wiper arm, is in essence a contact point that can be moved along the resistance. Thus, the resistance seen from one outer terminal to the wiper plus the resistance from the wiper to the other outer terminal will always equal the nominal resistance of the device. This three terminal configuration is used typically to adjust voltage via the voltage divider rule, hence the name potentiometer, or *pot* for short. While the resistance change is often linear with rotation (i.e., rotating the shaft 50% yields 50% resistance), other schemes, called *tapers*, are also found. One common non-linear taper is the logarithmic taper. It is important to note that linearity can be compromised (sometimes on purpose) if the resistance loading the potentiometer is not significantly larger in value than the potentiometer itself.

If only a single outer terminal and the wiper are used, the device is merely an adjustable resistor and is referred to as a rheostat. These may be placed in-line with a load to control the load current, the greater the resistance, the smaller the current.

### Equipment

- |                                  |             |           |
|----------------------------------|-------------|-----------|
| (1) Adjustable DC Power Supply   | model:_____ | srn:_____ |
| (1) Digital Multimeter           | model:_____ | srn:_____ |
| (1) 10 k $\Omega$ potentiometer  |             |           |
| (1) 100 k $\Omega$ potentiometer |             |           |
| (1) 1 k $\Omega$                 | _____       |           |
| (1) 4.7 k $\Omega$               | _____       |           |
| (1) 47 k $\Omega$                | _____       |           |

## Schematics

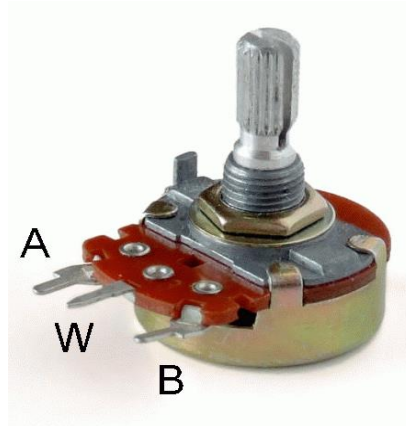


Figure 9.1

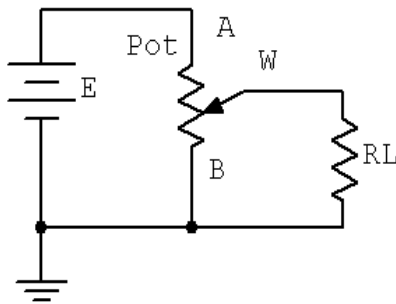


Figure 9.2

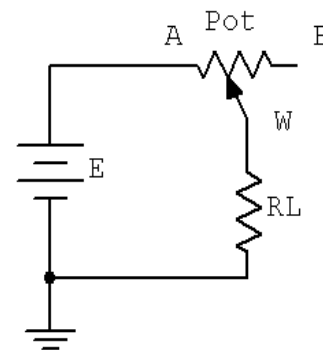


Figure 9.3

## Procedure

1. A typical potentiometer is shown in Figure 9.1. Using a 10 k pot, first rotate the knob fully counter-clockwise and using the DMM, measure the resistance from terminal A to the wiper arm, W. Then measure the value from the wiper arm to terminal B. Record these values in Table 9.1. Add the two readings, placing the result in the final column.
2. Rotate the knob 1/4 turn clockwise and repeat the measurements of step 1. Repeat this process for the remaining knob positions in Table 9.1. Note that the results of the final column should all equal the nominal value of the potentiometer.
3. Construct the circuit of Figure 9.2 using  $E = 10$  volts, a 10 k potentiometer and leave  $R_L$  open. Rotate the knob fully counter-clockwise and measure the voltage from the wiper to ground. Record this value in Table 9.2. Continue taking and recording voltages as the knob is rotated to the other four positions in Table 9.2.

4. Set  $R_L$  to 47 k and repeat step 3.
5. Set  $R_L$  to 4.7 k and repeat step 3.
6. Set  $R_L$  to 1 k and repeat step 3.
7. Using a linear grid, plot the voltages of Table 9.2 versus position. Note that there will be four curves created, one for each load, but place them on a single graph. Note how the variance of the load affects the linearity and control of the voltage.
8. Construct the circuit of Figure 9.3 using  $E = 10$  volts, a 100 k potentiometer and  $R_L = 1$  k. Rotate the knob fully counter-clockwise and measure the current through the load. Record this value in Table 9.3. Repeat this process for the remaining knob positions in Table 9.3.
9. Replace the load resistor with a 4.7 k and repeat step 8.

## Data Tables

Position	$R_{AW}$	$R_{WB}$	$R_{AW} + R_{WB}$
Fully CCW			
1/4			
1/2			
3/4			
Fully CW			

Table 9.1

Position	$V_{WB}$ Open	$V_{WB}$ 47k	$V_{WB}$ 4.7k	$V_{WB}$ 1k
Fully CCW				
1/4				
1/2				
3/4				
Fully CW				

Table 9.2

Position	$I_L$ 1k	$I_L$ 4.7k
Fully CCW		
1/4		
1/2		
3/4		
Fully CW		

Table 9.3

## Questions

1. In Table 9.1, does the total resistance always equal the nominal resistance of the potentiometer?
2. If the potentiometer used for Table 9.1 had a logarithmic taper, how would the values change?
3. In Table 9.2, is the load voltage always directly proportional to the knob position? Is the progression always linear?
4. Explain the variation of the four curves plotted in step 7.
5. In the final circuit, is the load current always proportional to the knob position? If the load was much smaller, say just a few hundred Ohms, would the minimum and maximum currents be much different from those in Table 9.3?
6. How could the circuit of Figure 9.3 be modified so that the maximum current could be set to a value higher than that achieved by the supply and load resistor alone?

# 10

## Superposition Theorem

### Objective

The objective of this exercise is to investigate the application of the superposition theorem to multiple DC source circuits in terms of both voltage and current measurements. Power calculations will also be examined.

### Theory Overview

The superposition theorem states that in a linear bilateral multi-source DC circuit, the current through or voltage across any particular element may be determined by considering the contribution of each source independently, with the remaining sources replaced with their internal resistance. The contributions are then summed, paying attention to polarities, to find the total value. Superposition cannot in general be applied to non-linear circuits or to non-linear functions such as power.

### Equipment

- |                                     |              |           |
|-------------------------------------|--------------|-----------|
| (1) Adjustable Dual DC Power Supply | model: _____ | sn: _____ |
| (1) Digital Multimeter              | model: _____ | sn: _____ |
| (1) 4.7 k $\Omega$                  | _____        |           |
| (1) 6.8 k $\Omega$                  | _____        |           |
| (1) 10 k $\Omega$                   | _____        |           |
| (1) 22 k $\Omega$                   | _____        |           |
| (1) 33 k $\Omega$                   | _____        |           |

### Schematics

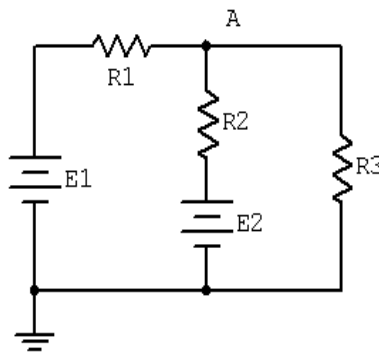


Figure 10.1



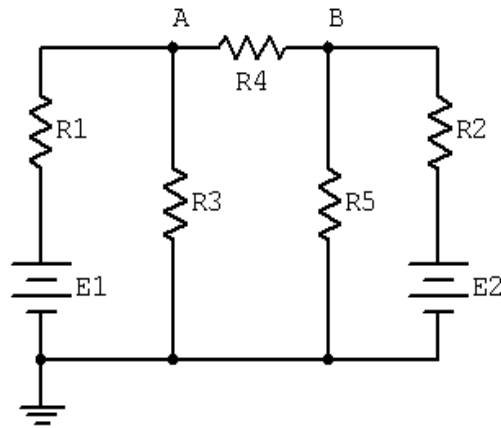


Figure 10.2

## Procedure

### Voltage Application

1. Consider the dual supply circuit of Figure 10.1 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k and  $R3 = 10$  k. To find the voltage from node A to ground, superposition may be used. Each source is considered by itself. First consider source E1 by assuming that E2 is replaced with its internal resistance (a short). Determine the voltage at node A using standard series-parallel techniques and record it in Table 10.1. Make sure to indicate the polarity. Repeat the process using E2 while shorting E1. Finally, sum these two voltages and record in Table 10.1.
2. To verify the superposition theorem, the process may be implemented directly by measuring the contributions. Build the circuit of Figure 10.1 with the values specified in step 1, however, replace E2 with a short. Do **not** simply place a shorting wire across source E2! This will overload the power supply.
3. Measure the voltage at node A and record in Table 10.1. Be sure to note the polarity.
4. Remove the shorting wire and insert source E2. Also, replace source E1 with a short. Measure the voltage at node A and record in Table 10.1. Be sure to note the polarity.
5. Remove the shorting wire and re-insert source E1. Both sources should now be in the circuit. Measure the voltage at node A and record in Table 10.1. Be sure to note the polarity. Determine and record the deviations between theory and experimental results.

### Current and Power Application

6. Consider the dual supply circuit of Figure 10.2 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k,  $R3 = 10$  k,  $R4 = 22$  k and  $R5 = 33$  k. To find the current through R4 flowing from node A to B,

superposition may be used. Each source is again treated independently with the remaining sources replaced with their internal resistances. Calculate the current through R4 first considering E1 and then considering E2. Sum these results and record the three values in Table 10.2.

7. Assemble the circuit of Figure 10.2 using the values specified. Replace source E2 with a short and measure the current through R4. Be sure to note the direction of flow and record the result in Table 10.2.
8. Replace the short with source E2 and swap source E1 with a short. Measure the current through R4. Be sure to note the direction of flow and record the result in Table 10.2.
9. Remove the shorting wire and re-insert source E1. Both sources should now be in the circuit. Measure the current through R4 and record in Table 10.2. Be sure to note the direction. Determine and record the deviations between theory and experimental results.
10. Power is not a linear function as it is proportional to the square of either voltage or current. Consequently, superposition should not yield an accurate result when applied directly to power. Based on the measured currents in Table 10.2, calculate the power in R4 using E1-only and E2-only and record the values in Table 10.3. Adding these two powers yields the power as predicted by superposition. Determine this value and record it in Table 10.3. The true power in R4 may be determined from the total measured current flowing through it. Using the experimental current measured when both E1 and E2 were active (Table 10.2), determine the power in R4 and record it in Table 10.3.

## Multisim

11. Build the circuit of Figure 10.2 in Multisim. Using the virtual DMM as an ammeter, determine the current through resistor R4 and compare it to the theoretical and measured values recorded in Table 10.2.

## Data Tables

Source	V <sub>A</sub> Theory	V <sub>A</sub> Experimental	Deviation
E1 Only			
E2 Only			
E1 and E2			

Table 10.1

Source	$I_{R4}$ Theory	$I_{R4}$ Experimental	Deviation
E1 Only			
E2 Only			
E1 and E2			

Table 10.2

Source	$P_{R4}$
E1 Only	
E2 Only	
E1 + E2	
E1 and E2	

Table 10.3

## Questions

1. Based on the results of Tables 10.1, 10.2 and 10.3, can superposition be applied successfully to voltage, current and power levels in a DC circuit?
2. If one of the sources in Figure 10.1 had been inserted with the opposite polarity, would there be a significant change in the resulting voltage at node A? Could both the magnitude and polarity change?
3. If both of the sources in Figure 10.1 had been inserted with the opposite polarity, would there be a significant change in the resulting voltage at node A? Could both the magnitude and polarity change?
4. Why is it important to note the polarities of the measured voltages and currents?

# 11

## Thevenin's Theorem

### Objective

The objective of this exercise is to examine the use of Thevenin's Theorem to create simpler versions of DC circuits as an aide to analysis. Multiple methods of experimentally obtaining the Thevenin resistance will be explored.

### Theory Overview

Thevenin's Theorem for DC circuits states that any two port linear network may be replaced by a single voltage source with an appropriate internal resistance. The Thevenin equivalent will produce the same load current and voltage as the original circuit to any load. Consequently, if many different loads or sub-circuits are under consideration, using a Thevenin equivalent may prove to be a quicker analysis route than "reinventing the wheel" each time.

The Thevenin voltage is found by determining the open circuit output voltage. The Thevenin resistance is found by replacing any DC sources with their internal resistances and determining the resulting combined resistance as seen from the two ports using standard series-parallel analysis techniques. In the laboratory, the Thevenin resistance may be found using an ohmmeter (again, replacing the sources with their internal resistances) or by using the matched load technique. The matched load technique involves replacing the load with a variable resistance and then adjusting it until the load voltage is precisely one half of the unloaded voltage. This would imply that the other half of the voltage must be dropped across the equivalent Thevenin resistance, and as the Thevenin circuit is a simple series loop then the two resistances must be equal as they have identical currents and voltages.

### Equipment

- |   |                       |
|---|-----------------------|
| (1) Adjustable DC Power Supply                  | model:_____ srn:_____ |
| (1) Digital Multimeter                          | model:_____ srn:_____ |
| (1) 2.2 k $\Omega$                              | _____                 |
| (1) 3.3 k $\Omega$                              | _____                 |
| (1) 4.7 k $\Omega$                              | _____                 |
| (1) 6.8 k $\Omega$                              | _____                 |
| (1) 8.2 k $\Omega$                              | _____                 |
| (1) 10 k potentiometer or resistance decade box |                       |

## Schematics

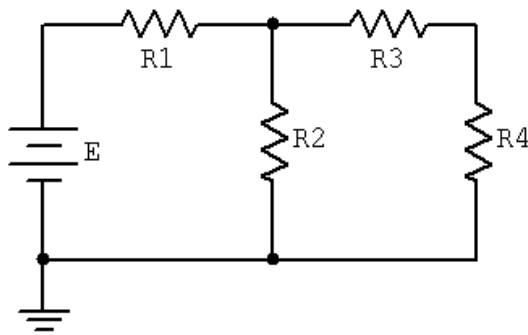


Figure 11.1

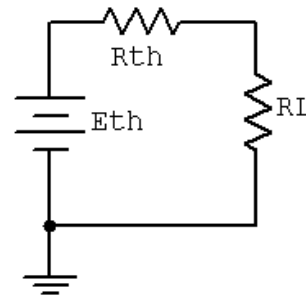


Figure 11.2

## Procedure

1. Consider the circuit of Figure 11.1 using  $E = 10$  volts,  $R1 = 3.3$  k,  $R2 = 6.8$  k,  $R3 = 4.7$  k and  $R4$  ( $R_{Load}$ ) = 8.2 k. This circuit may be analyzed using standard series-parallel techniques. Determine the voltage across the load,  $R4$ , and record it in Table 11.1. Repeat the process using 2.2 k for  $R4$ .
2. Build the circuit of Figure 11.1 using the values specified in step one, with  $R_{Load} = 8.2$  k. Measure the load voltage and record it in Table 11.1. Repeat this with a 2.2 k load resistance. Determine and record the deviations. Do not deconstruct the circuit.
3. Determine the theoretical Thevenin voltage of the circuit of Figure 11.1 by finding the open circuit output voltage. That is, replace the load with an open and calculate the voltage produced between the two open terminals. Record this voltage in Table 11.2.
4. To calculate the theoretical Thevenin resistance, first remove the load and then replace the source with its internal resistance (ideally, a short). Finally, determine the combination series-parallel resistance as seen from the where the load used to be. Record this resistance in Table 11.2.
5. The experimental Thevenin voltage maybe determined by measuring the open circuit output voltage. Simply remove the load from the circuit of step one and then replace it with a voltmeter. Record this value in Table 11.2.
6. There are two methods to measure the experimental Thevenin resistance. For the first method, using the circuit of step one, replace the source with a short. Then replace the load with the ohmmeter. The Thevenin resistance may now be measured directly. Record this value in Table 11.2.
7. In powered circuits, ohmmeters are not effective while power is applied. An alternate method relies on measuring the effect of the load resistance. Return the voltage source to the circuit, replacing the short from step six. For the load, insert either the decade box or the potentiometer. Adjust this device until the load voltage is half of the open circuit voltage measured in step five and record in Table 11.2

under “Method 2”. At this point, the load and the Thevenin resistance form a simple series loop as seen in Figure 11.2. This means that they “see” the same current. If the load exhibits one half of the Thevenin voltage then the other half must be dropped across the Thevenin resistance, that is  $V_{RL} = V_{RTH}$ . Consequently, the resistances have the same voltage and current, and therefore must have the same resistance according to Ohm’s Law.

8. Consider the Thevenin equivalent of Figure 11.2 using the theoretical  $E_{TH}$  and  $R_{TH}$  from Table 11.2 along with 8.2 k for the load (RL). Calculate the load voltage and record it in Table 11.3. Repeat the process for a 2.2 k load.
9. Build the circuit of Figure 11.2 using the measured  $E_{TH}$  and  $R_{TH}$  from Table 11.2 along with 8.2 k for the load (RL). Measure the load voltage and record it in Table 11.3. Also determine and record the deviation.
10. Repeat step nine using a 2.2 k load.

## Data Tables

### Original Circuit

$R_4$ (Load)	$V_{Load}$ Theory	$V_{Load}$ Experimental	Deviation
8.2 k			
2.2 k			

Table 11.1

### Thevenized Circuit

	Theory	Experimental
$E_{TH}$		
$R_{TH}$		
$R_{TH}$ Method 2	X	

Table 11.2

$R_4$ (Load)	$V_{\text{Load}}$ Theory	$V_{\text{Load}}$ Experimental	Deviation
8.2 k			
2.2 k			

Table 11.3

## Questions

1. Do the load voltages for the original and Thevenized circuits match for both loads? Is it logical that this could be extended to any arbitrary load resistance value?
2. Assuming several loads were under consideration, which is faster, analyzing each load with the original circuit of Figure 11.1 or analyzing each load with the Thevenin equivalent of Figure 11.2?
3. How would the Thevenin equivalent computations change if the original circuit contained more than one voltage source?

# 12

## Maximum Power Transfer

### Objective

The objective of this exercise is to determine the conditions under which a load will produce maximum power. Further, the variance of load power and system efficiency will be examined graphically.

### Theory Overview

In order to achieve the maximum load power in a DC circuit, the load resistance must equal the driving resistance, that is, the internal resistance of the source. Any load resistance value above or below this will produce a smaller load power. System efficiency ( $\eta$ ) is 50% at the maximum power case. This is because the load and the internal resistance form a basic series loop, and as they have the same value, they must exhibit equal currents and voltages, and hence equal powers. As the load increases in resistance beyond the maximizing value the load voltage will rise, however, the load current will drop by a greater amount yielding a lower load power. Although this is not the maximum load power, this will represent a larger percentage of total power produced, and thus a greater efficiency (the ratio of load power to total power).

### Equipment

(1) Adjustable DC Power Supply

model: \_\_\_\_\_ sn: \_\_\_\_\_

(1) Digital Multimeter

model: \_\_\_\_\_ sn: \_\_\_\_\_

(1) 3.3 k $\Omega$  \_\_\_\_\_

(1) Resistance Decade Box

### Schematics

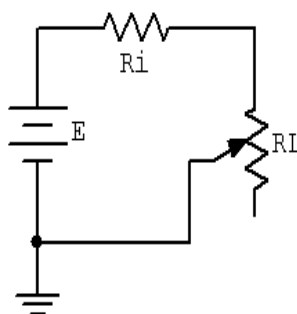


Figure 12.1



## Procedure

1. Consider the simple the series circuit of Figure 12.1 using  $E = 10$  volts and  $R_i = 3.3$  k.  $R_i$  forms a simple voltage divider with  $R_L$ . The power in the load is  $V_L^2/R_L$  and the total circuit power is  $E^2/(R_i+R_L)$ . The larger the value of  $R_L$ , the greater the load voltage, however, this does not mean that very large values of  $R_L$  will produce maximum load power due to the division by  $R_L$ . That is, at some point  $V_L^2$  will grow more slowly than  $R_L$  itself. This crossover point should occur when  $R_L$  is equal to  $R_i$ . Further, note that as  $R_L$  increases, total circuit power decreases due to increasing total resistance. This should lead to an increase in efficiency. An alternate way of looking at the efficiency question is to note that as  $R_L$  increases, circuit current decreases. As power is directly proportional to the square of current, as  $R_L$  increases the power in  $R_i$  must decrease leaving a larger percentage of total power going to  $R_L$ .
2. Using  $R_L = 30$ , compute the expected values for load voltage, load power, total power and efficiency, and record them in Table 12.1. Repeat for the remaining  $R_L$  values in the Table. For the middle entry labeled ACTUAL, insert the measured value of the 3.3 k used for  $R_i$ .
3. Build the circuit of Figure 12.1 using  $E = 10$  volts and  $R_i = 3.3$  k. Use the decade box for  $R_L$  and set it to 30 Ohms. Measure the load voltage and record it in Table 12.2. Calculate the load power, total power and efficiency, and record these values in Table 12.2. Repeat for the remaining resistor values in the table.
4. Create two plots of the load power versus the load resistance value using the data from the two tables, one for theoretical, one for experimental. For best results make sure that the horizontal axis ( $R_L$ ) uses a log scaling instead of linear.
5. Create two plots of the efficiency versus the load resistance value using the data from the two tables, one for theoretical, one for experimental. For best results make sure that the horizontal axis ( $R_L$ ) uses a log scaling instead of linear.

## Data Tables

$R_L$	$V_L$	$P_L$	$P_T$	$\eta$
30				
150				
500				
1 k				
2.5 k				
Actual=				
4 k				
10 k				
25 k				
70 k				
300 k				

Table 12.1

$R_L$	$V_L$	$P_L$	$P_T$	$\eta$
30				
150				
500				
1 k				
2.5 k				
Actual=				
4 k				
10 k				
25 k				
70 k				
300 k				

Table 12.2

## Questions

1. At what point does maximum load power occur?
2. At what point does maximum total power occur?
3. At what point does maximum efficiency occur?
4. Is it safe to assume that generation of maximum load power is always a desired goal? Why/why not?

# 13

## Mesh Analysis

### Objective

The study of mesh analysis is the objective of this exercise, specifically its usage in multi-source DC circuits. Its application to finding circuit currents and voltages will be investigated.

### Theory Overview

Multi-source DC circuits may be analyzed using a mesh current technique. The process involves identifying a minimum number of small loops such that every component exists in at least one loop. Kirchhoff's Voltage Law is then applied to each loop. The loop currents are referred to as mesh currents as each current interlocks or meshes with the surrounding loop currents. As a result there will be a set of simultaneous equations created, an unknown mesh current for each loop. Once the mesh currents are determined, various branch currents and component voltages may be derived.

### Equipment

- |                                |                        |
|--------------------------------|------------------------|
| (1) Adjustable DC Power Supply | model: _____ sm: _____ |
| (1) Digital Multimeter         | model: _____ sm: _____ |
| (1) 4.7 k $\Omega$             | _____                  |
| (1) 6.8 k $\Omega$             | _____                  |
| (1) 10 k $\Omega$              | _____                  |
| (1) 22 k $\Omega$              | _____                  |
| (1) 33 k $\Omega$              | _____                  |

### Schematics

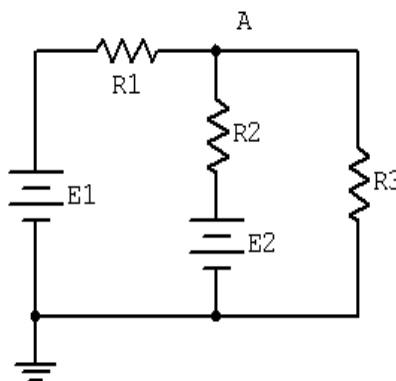


Figure 13.1

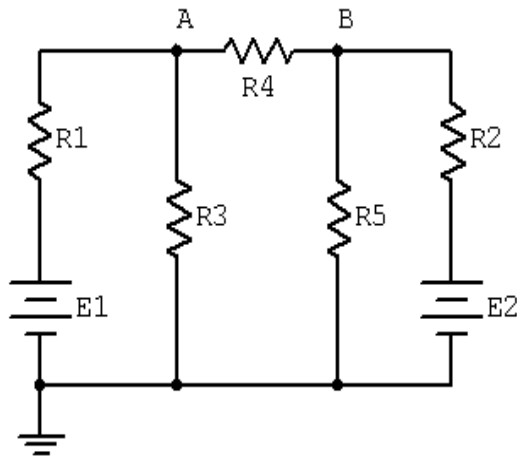


Figure 13.2

## Procedure

1. Consider the dual supply circuit of Figure 13.1 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k and  $R3 = 10$  k. To find the voltage from node A to ground, mesh analysis may be used. This circuit may be described via two mesh currents, loop one formed with  $E1$ ,  $R1$ ,  $R2$  and  $E2$ , and loop two formed with  $E2$ ,  $R2$  and  $R3$ . Note that these mesh currents are the currents flowing through  $R1$  and  $R3$  respectively.
2. Using KVL, write the loop expressions for these two loops and then solve to find the mesh currents. Note that the third branch current (that of  $R2$ ) is the combination of the mesh currents and that the voltage at node A can be determined using the second mesh current and Ohm's Law. Compute these values and record them in Table 13.1.
3. Build the circuit of Figure 13.1 using the values specified in step one. Measure the three branch currents and the voltage at node A and record in Table 13.1. Be sure to note the directions and polarities. Finally, determine and record the deviations in Table 13.1.
4. Consider the dual supply circuit of Figure 13.2 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k,  $R3 = 10$  k,  $R4 = 22$  k and  $R5 = 33$  k. This circuit will require three loops to describe fully. This means that there will be three mesh currents in spite of the fact that there are five branch currents. The three mesh currents correspond to the currents through  $R1$ ,  $R2$ , and  $R4$ .
5. Using KVL, write the loop expressions for these loops and then solve to find the mesh currents. Note that the voltages at nodes A and B can be determined using the mesh currents and Ohm's Law. Compute these values and record them in Table 13.2.

- Build the circuit of Figure 13.2 using the values specified in step four. Measure the three mesh currents and the voltages at node A, node B, and from node A to B, and record in Table 13.2. Be sure to note the directions and polarities. Finally, determine and record the deviations in Table 13.2.

## Data Tables

Parameter	Theory	Experimental	Deviation
$I_{R1}$			
$I_{R2}$			
$I_{R3}$			
$V_A$			

Table 13.1

Parameter	Theory	Experimental	Deviation
$I_{R1}$			
$I_{R2}$			
$I_{R4}$			
$V_A$			
$V_B$			
$V_{AB}$			

Table 13.2

## Questions

- Do the polarities of the sources in Figure 13.1 matter as to the resulting currents? Will the magnitudes of the currents be the same if one or both sources have an inverted polarity?

2. In both circuits of this exercise the negative terminals of the sources are connected to ground. Is this a requirement for mesh analysis? What would happen to the mesh currents if the positions of E1 and R1 in Figure 13.1 were swapped?
  
3. If branch current analysis (BCA) was applied to the circuit of Figure 13.2, how many unknown currents would have to be analyzed and how many equations would be needed? How does this compare to mesh analysis?
  
4. The circuits of Figures 13.1 and 13.2 had been analyzed previously in the Superposition Theorem exercise. How do the results of this exercise compare to the earlier results? Should the resulting currents and voltages be identical? If not, what sort of things might affect the outcome?

# 14

## Nodal Analysis

### Objective

The study of nodal analysis is the objective of this exercise, specifically its usage in multi-source DC circuits. Its application to finding circuit currents and voltages will be investigated.

### Theory Overview

Multi-source DC circuits may be analyzed using a node voltage technique. The process involves identifying all of the circuit nodes, a node being a point where various branch currents combine. A reference node, usually ground, is included. Kirchhoff's Current Law is then applied to each node. Consequently a set of simultaneous equations are created with an unknown voltage for each node with the exception of the reference. In other words, a circuit with a total of five nodes including the reference will yield four unknown node voltages and four equations. Once the node voltages are determined, various branch currents and component voltages may be derived.

### Equipment

(1) Adjustable DC Power Supply	model: _____	srn: _____
(1) Digital Multimeter	model: _____	srn: _____
(1) 4.7 k $\Omega$	_____	
(1) 6.8 k $\Omega$	_____	
(1) 10 k $\Omega$	_____	
(1) 22 k $\Omega$	_____	
(1) 33 k $\Omega$	_____	



## Schematics

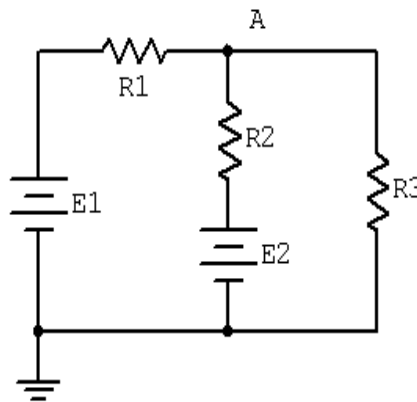


Figure 14.1

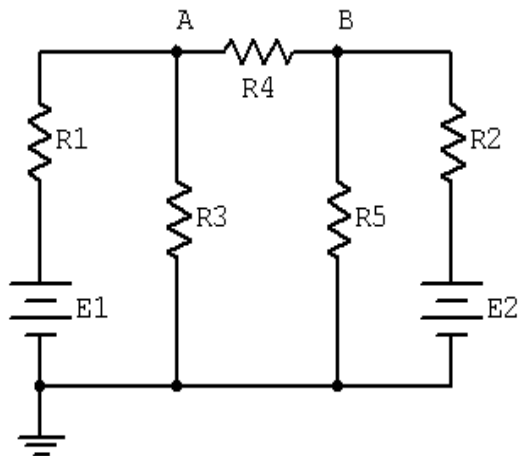


Figure 14.2

## Procedure

1. Consider the dual supply circuit of Figure 14.1 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k and  $R3 = 10$  k. To find the voltage from node A to ground, nodal analysis may be applied. In this circuit note that there is only one node and therefore only one equation with one unknown is needed. Once this potential is found, all other circuit currents and voltages may be found by applying Ohm's Law and/or KVL and KCL.
2. Write the node equation for the circuit of Figure 14.1 and solve for node voltage A. Also, determine the current through  $R3$ . Record these values in Table 14.1.

3. Construct the circuit of Figure 14.1 using the values specified in step one. Measure the voltage from node A to ground along with the current through R3. Record these values in Table 14.1. Also determine and record the deviations.
4. Consider the dual supply circuit of Figure 14.2 using  $E_1 = 10$  volts,  $E_2 = 15$  volts,  $R_1 = 4.7$  k,  $R_2 = 6.8$  k,  $R_3 = 10$  k,  $R_4 = 22$  k and  $R_5 = 33$  k. Applying nodal analysis to this circuit yields two equations with two unknowns, namely node voltages A and B. Again, once these potentials are found, any other circuit current or voltage may be determined by applying Ohm's Law and/or KVL and KCL.
5. Write the node equations for the circuit of Figure 14.2 and solve for node voltage A, node voltage B and the potential from A to B. Also, determine the current through R4. Record these values in Table 14.2.
6. Construct the circuit of Figure 14.2 using the values specified in step four. Measure the voltages from node A to ground, node B to ground and from node A to B, along with the current through R4. Record these values in Table 14.2. Also determine and record the deviations.

## Multisim

7. Build the circuit of Figure 14.2 in Multisim. Using the DC Operating Point simulation function, determine the voltages at nodes A and B, and compare these to the theoretical and measured values recorded in Table 14.2.

## Data Tables

Parameter	Theory	Experimental	Deviation
$V_A$			
$I_{R3}$			

Table 14.1

Parameter	Theory	Experimental	Deviation
$V_A$			
$V_B$			
$V_{AB}$			
$I_{R4}$			

Table 14.2

## Questions

1. Do the polarities of the sources in Figure 14.1 matter as to the resulting voltages? Will the magnitudes of the voltages be the same if one or both sources have an inverted polarity?
2. In both circuits of this exercise the negative terminals of the sources are connected to ground. Is this a requirement for nodal analysis? What would happen to the node voltages if the positions of  $E_1$  and  $R_1$  in Figure 14.1 were swapped?
3. If mesh analysis was applied to the circuit of Figure 14.2, how many unknown currents would have to be analyzed and how many equations would be needed? How does this compare to nodal analysis?
4. The circuits of Figures 14.1 and 14.2 had been analyzed previously in the Superposition Theorem and Mesh Analysis exercises. How do the results of this exercise compare to the earlier results? Should the resulting currents and voltages be identical? If not, what sort of things might affect the outcome?
5. In general, compare and contrast the application of Superposition, Mesh and Nodal Analyses to multi-source DC circuits. What are the advantages and disadvantages of each? Are some circuits better approached with a particular technique? Will each technique enable any particular current or voltage to be found or are there limitations?

# 15

## Capacitors and Inductors

### Objective

The objective of this exercise is to become familiar with the basic behavior of capacitors and inductors. This includes determination of the equivalent of series and parallel combinations of each, the division of voltage among capacitors in series, and the steady state behavior of simple RLC circuits.

### Theory Overview

The inductor behaves identically to the resistor in terms of series and parallel combinations. That is, the equivalent of a series connection of inductors is simply the sum of the values. For a parallel connection of inductors either the product-sum rule or the “reciprocal of the sum of the reciprocals” rule may be used. Capacitors, in contrast, behave in an opposite manner. The equivalent of a parallel grouping of capacitors is simply the sum of the capacitances while a series connection must be treated with the product-sum or reciprocal rules.

For circuit analysis in the steady state case, inductors may be treated as shorts (or for more accuracy, as a small resistance known as the coil resistance,  $R_{\text{coil}}$ , which is dependent on the construction of the device) while capacitors may be treated as opens. If multiple capacitors are in series, the applied voltage will be split among them inversely to the capacitance. That is, the largest capacitors will drop the smallest voltages.

### Equipment

(1) Adjustable DC Power Supply	model:_____	sn:_____
(1) Digital Multimeter	model:_____	sn:_____
(1) 4.7 k $\Omega$	_____	
(1) 10 k $\Omega$	_____	
(1) .1 $\mu\text{F}$	_____	
(1) .22 $\mu\text{F}$	_____	
(1) 1 mH	_____	
(1) 10 mH	_____	

## Schematics

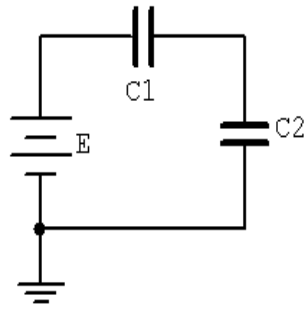


Figure 15.1

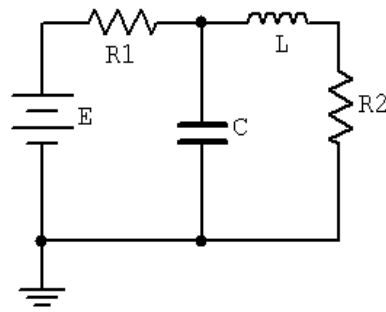


Figure 15.2

## Procedure

1. Using an RLC meter, measure the values of the two capacitors and two inductors and record them in Table 15.1. Also, measure the equivalent DC series resistance of the two inductors and record them in Table 15.1. Using these values, determine and record the theoretical series and parallel combinations specified in Table 15.2.
2. Connect the two capacitors in series and measure the total capacitance using the RLC meter. Record this value in Table 15.2. Repeat this process for the remaining combinations in Table 15.2. Also determine and record the deviations.
3. Consider the circuit of Figure 15.1 using  $E = 5$  volts,  $C1 = .1 \mu\text{F}$  and  $C2 = .22 \mu\text{F}$ . Determine the voltage across each capacitor and record these values in Table 15.3.
4. Build the circuit of Figure 15.1 using  $E = 5$  volts,  $C1 = .1 \mu\text{F}$  and  $C2 = .22 \mu\text{F}$ . Measure the voltage across each capacitor and record these values in Table 15.3. Also determine and record the deviations.
5. Consider the circuit of Figure 15.2 using  $E = 10$  volts,  $R1 = 4.7 \text{ k}$ ,  $R2 = 10 \text{ k}$ ,  $C = .1 \mu\text{F}$  and  $L = 1 \text{ mH}$ . Determine the steady state voltage across each component and record these values in Table 15.4.
6. Build the circuit of Figure 15.2 using  $E = 10$  volts,  $R1 = 4.7 \text{ k}$ ,  $R2 = 10 \text{ k}$ ,  $C = .1 \mu\text{F}$  and  $L = 1 \text{ mH}$ . Energize the circuit. It will reach steady state in less than one second. Measure the steady state voltage across each component and record these values in Table 15.4. Also determine and record the deviations.

## Data Tables

### Series and Parallel Combinations

Component	Experimental	$R_{\text{coil}}$
.1 $\mu\text{F}$		X
.22 $\mu\text{F}$		X
1 mH		
10 mH		

Table 15.1

Pairing	Theory	Experimental	Deviation
.1 $\mu\text{F}$ series .22 $\mu\text{F}$			
.1 $\mu\text{F}$ parallel .22 $\mu\text{F}$			
1 mH series 10 mH			
1 mH parallel 10 mH			

Table 15.2

### Capacitive Series Circuit

Voltage	Theory	Experimental	Deviation
$V_{C1}$			
$V_{C2}$			

Table 15.3

## Steady State RLC Circuit

Voltage	Theory	Experimental	Deviation
$V_{R1}$			
$V_{R2}$			
$V_C$			
$V_L$			

Table 15.4

## Questions

1. Does the value of  $R_{\text{coil}}$  appear to be correlated with the inductance value?
2. How do capacitors and inductors in series and in parallel compare with resistors?
3. In a series combination of capacitors, how does the voltage divide up?
4. For DC steady state analysis, what can be said about capacitors and inductors?
5. Does the value of  $R_{\text{coil}}$  seem to have much impact on the final circuit? Why/why not?

## Appendix A: Technical Report Guidelines

It is essential that individuals be able to express their ideas and defend their arguments with clarity, detail and subtlety. Similarly, it is important that they can read and critique the ideas and arguments of others in like manner. The creation of lab reports assists in this endeavor. All reports should be neat and legible. Standard technical writing style is expected along with proper grammar and spelling. This means that active voice, first person, personal pronouns, and the like should be avoided. For example, don't write "I set the power supply to 6 volts". Instead use "The power supply was set to 6 volts". **Reports are an individual endeavor.** Although it is perfectly fine to discuss your data and experimental results with your lab partner, the creation of the report itself is an individual exercise. Plagiarism will not be tolerated. A **formal report** should conform to the following outline, in the order given:

1. **Cover page.** Title, date, your name, partners name.
2. **Objective (AKA Hypothesis).** Answer the question "What are you trying to show/verify?" These are statements of the items that you are investigating in this particular exercise.
3. **Conclusion.** Answer the question "What was shown/verified?" These are concise statements of fact regarding the circuit action(s) under investigation. Make sure that you have moved from the *specific lab situation* to the *general case*. If all works well, these should match nicely with your Objective section. Under no circumstances should you reach a conclusion that is not supported by your data, even if that conclusion is stated in the text or in lecture. What matters here is what **you** did and your analysis of it. If there is a discrepancy between your results and theory, state the discrepancy and **don't** ignore your results.
4. **Discussion (AKA Analysis).** Reduce and analyze your data. Explain circuit action or concepts under investigation. Relate theoretical results to the lab results. Don't just state *what* happened, but comment on *why* and its implications. Derive your conclusions from this section. Any deviations from the given procedure (lab manual or handout) must be noted in this section. The Discussion is the penultimate part that you write.
5. **Diagrams** with actual/nominal values. Do not sketch these. Use a CAD program such as Multisim or appropriate drawing templates.
6. **Equipment List.** Include model and serial numbers.
7. **Final Data Sheet.** Include all derived and calculated data. Make sure that you include percent deviations for each theory/measurement pair. Use Percent Deviation = (Measured-Theory)/Theory \* 100, and include the sign.
8. **Original Data Sheet.** Include actual measured values.
9. **Sample Calculations.** The key here is *sample*. Show the formulas used, values inserted, and final answers.



10. **Graphs, Answers to questions at the end of the exercise, Other.** All graphs must be properly titled, created using appropriate scales, and identified with labels. It is suggested that graphs be created with a plotting program or a spreadsheet. Alternately, graphs may be created manually but must be drawn using either a straight edge or a french curve (depending on the type of graph) on appropriate graph paper.

**Non-formal reports should include items 2, 3, 4, 7 and 10.** You can place the normal cover page info at the top of the first page.

Make sure that you leave sufficient space in the margins and between sections for my comments. Either 1.5 or double line spacing is fine. Multi-page reports must be stapled in the upper left corner. Paper clips, fold-overs, bits of hook-up wire, etc. are not acceptable. Below is the grading standard.

**Grade of A:** The report meets or exceeds the assignment particulars. The report is neat and professional in appearance, including proper spelling and syntax. The analysis is at the appropriate level and of sufficient detail. Data tables and graphical data are presented in a clear and concise manner. Problem solutions are sufficiently detailed and correct. Diagrams have a professional appearance.

**Grade of B:** The report is close to the ideal although it suffers from some minor drawbacks which may include some spelling or grammatical errors, analyses which may lack sufficient detail, minor omissions in tabular or graphical data, and the like. In general, the report is solid but could use refinement or tightening.

**Grade of C:** The report is serviceable and conveys the major ideas although it may be vague in spots. Spelling and grammatical errors may be more numerous than those found in a grade A or B report. Some gaps in data or omissions in explanations may be seen.

**Grade of D:** Besides typical spelling and grammatical errors, the report suffers from logical errors such as conclusions which are not supported by laboratory data. Analyses tend to be vague and possibly misleading. Graphs and diagrams are drawn in an unclear manner.

**Grade of F:** The report exhibits many of the following deficiencies: Excessive spelling and grammatical errors, missing sections such as graphs, tables, and analyses, blatantly incorrect analyses, wayward or incomprehensible data, problem solutions tend to be incorrect or missing, and graphical data or diagrams are presented in a shoddy manner.

## Appendix B: An Example Technical Report

What follows, starting on the next page, is an example of a technical laboratory report. Read the example *after* reading the report guidelines above. This uses the **non-formal** style.

The experiment in question is completely fabricated, but the report will illustrate both the expected form and content. The mock experiment involves measuring the speed of sound in various materials and whether or not this speed is affected by temperature. In this exercise, the experimenter has affixed small transducers to each end of a solid bar of the material under investigation (rather like a small loudspeaker and microphone). A pulse is then applied to one end and a timer is used to determine how long it takes for the wave to reach the other end. Knowing the length of the bar, the velocity may be computed. The bars are then heated to different temperatures and the process repeated to see if the velocity changes. Appropriate tables and graphs are presented.

The report uses 12 point Times Roman font with 1.5 line spacing although 11 or even 10 point may be preferred. There is no reason to “get fancy” with the appearance of the report. In fact, this will only serve as a distraction. Sufficient space is left for the instructor to insert comments. The length of any specific report can vary greatly depending on the amount of data recorded, the depth of analysis, added graphs, and the like.

As is sometimes the case, this mock experiment didn’t work perfectly.

## Speed of Sound in Various Materials

Science of Stuff, ET301

February 30, 2112

Name: Johan Bruhaus

Partner: Gail Faux

### Objective

The hypothesis investigated in this exercise is straight-forward, namely that the speed of propagation of sound depends on the characteristics of the material and that it may be affected by temperature. Three different materials will be investigated, each at three different temperatures. It is expected that the velocity in all three materials will be significantly greater than the velocity of sound in air (343 meters per second).

### Conclusion

The speed of sound in a particular material depends on the internal characteristics of the material. The speed may either increase or decrease with temperature. The velocity at room temperature for the SB alloy was approximately 2001 meters per second with a temperature coefficient (TC) of .01%. The GA alloy was 3050 meters per second with -.2% TC, and the CCCD material was measured at 997 meters per second with .1% TC. All values were within a few percent of those predicted by theory, and all velocities were clearly much greater than the velocity of sound in air.

### Discussion

To investigate the speed of sound, three bars of material, each one meter long, were obtained. The first was “Sonic Bronze” or SB, an alloy of tin, copper, zinc, and porcupinium. The second material, “Green Aluminum” or GA, is an alloy of aluminum and kryptonite, while the third, CCCD, is commonly known as “Chocolate Chip Cookie Dough”.

An acoustical transducer was attached to each end of the bar under investigation. A pulse was applied to one end and a digital timer was used to determine how long it took for the wave to travel down the bar to the pickup transducer. As each bar was one meter long, the velocity in meters per second is simply  $1/\text{time delay}$ . The bar was then placed in an industrial oven and the

measurement repeated at temperatures of 75C and 125C to compare to the nominal room temperature (25C) results.

The room temperature results agreed strongly with the published data of the three materials. Comparing Table 1.1 to the 25C column of Table 1.2 showed a deviation no worse than 1.64% (final column, Table 1.2). The variation between materials is approximately 3:1, indicating how strongly the internal characteristics of the material influence the speed of propagation. The CCCD material, being the most plastic, should have the greatest internal frictional losses, and thus, the slowest velocity of the group. This was the case. The inclusion of porcupinium in the SB alloy was responsible for the modest velocity of this material. The waves have to propagate relatively slowly through the porcupinium compared to the GA alloy which is free of this ingredient. The speed of propagation for all materials was significantly faster than the speed of sound through air. Even the slowest of the group, CCCD, exhibited a velocity nearly three times that of air.

The temperature coefficients also showed tight agreement, and appear to be within just a few percent of the established values. Generally, the velocity increases with temperature, although the GA alloy produced the opposite affect. It is assumed that the inclusion of kryptonite in the alloy may be responsible for this. See Graph 1.1 for details.

There was a practical issue involving the CCCD material. The measurements at 25C and 75C were satisfactory, however, when the CCCD bar was removed from the 125C oven it had changed texture and color to a crispy golden brown and produced a strong, pleasing odor. Consequently, one member of the lab group ate approximately 10 centimeters of the bar before the velocity could be measured. To correct for this, the measured time delay was adjusted by a factor of 1.11 as the bar had been reduced to 90% of its original length.


## Data

Material	Velocity (m/s)	Temperature Coefficient (% change per degree C)
SB	2000	.01
GA	3000	-.21
CCCD	1000	.105

Table 1.1  
Published Theoretical Velocities and TC

Material	Velocity 25C (m/s)	Velocity 75C (m/s)	Velocity 125C (m/s)	Temperature Coefficient	%Deviation at 25C
SB	2001	2010	2021	.01	.05
GA	3050	2750	2440	-.2	1.64
CCCD	997	1049	1097*	.1	-.3

Table 1.2  
Experimental Velocities and TC  
\* See Discussion for explanation

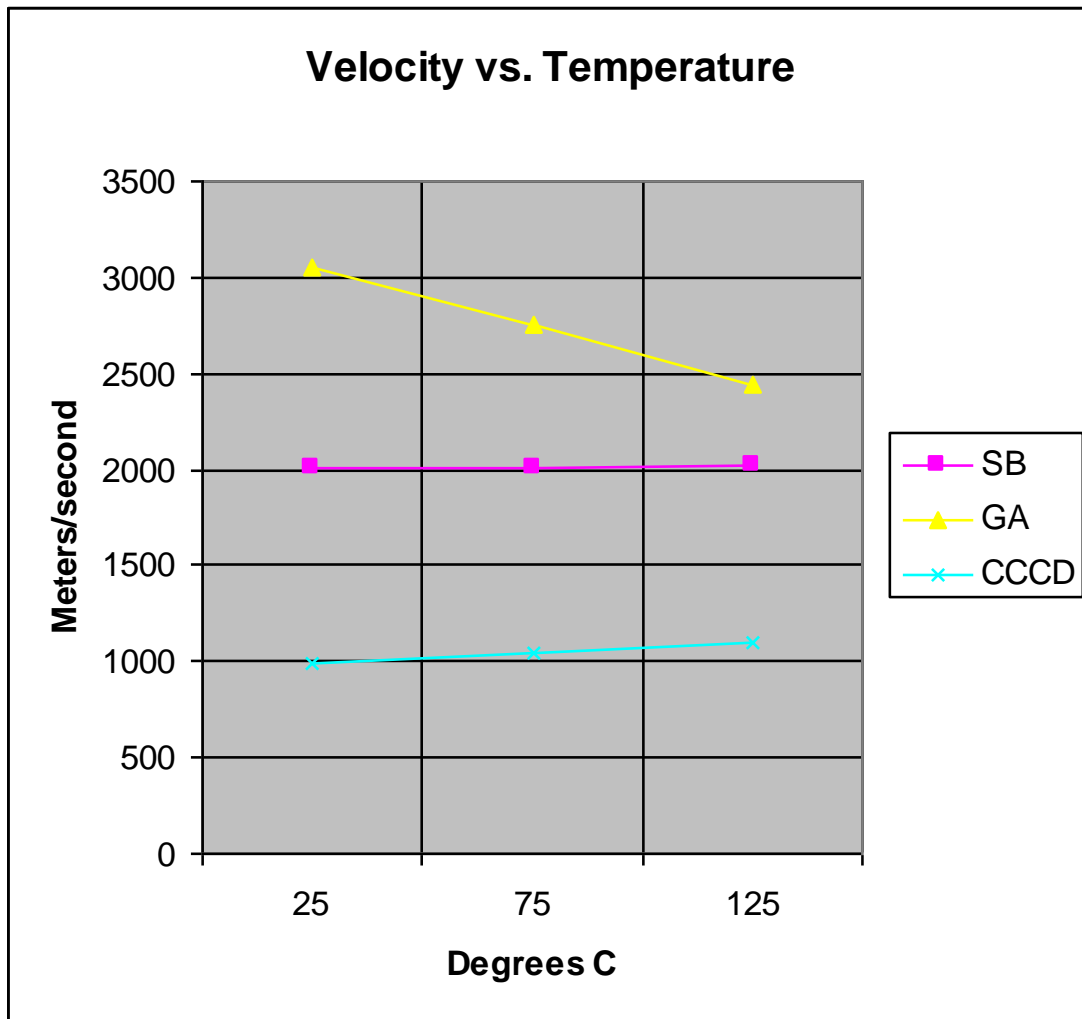

Graph 1.1

Variation of Velocity with Temperature, by Material

### Answers to Exercise Questions

1. *Is the velocity of sound unaffected by temperature?*

No. Graph 1.1 shows that in some cases (SB and CCCD) the velocity is directly proportional to temperature although it may be inversely proportional (GA).

2. *If the CCCD material had also been subjected to 175C, what would you expect?*

It is unlikely that a velocity at 175C could have been measured as the entire bar probably would have been consumed by the lab team before the transducers could be applied.

## Appendix C: Creating Graphs Using a Spreadsheet

While nothing beats good data plotting and analysis software (check out [SciDAVis](#) for an excellent free program), you can also create a variety of graphs using spreadsheets such as the one in [Open Office](#) or Excel (Microsoft Office). What follows works for Excel 2007 and Open Office 4. Other versions may have different menus and options. Here's how to take your tabular data from lab and create a graph. These instructions assume you will set the independent axis on the horizontal and the dependent axis as the vertical. This is the typical case but there are exceptions (see note at end). Remember, the independent axis presents the input parameter you set (e.g., a power supply voltage or a mass) and the dependent axis presents the output parameter (i.e., the item you are interested in and have measured as an outcome such as a resulting current or change in position).

1. Open a new worksheet. In the first column (column A), enter the text for the legend. This is particularly important if you're plotting multiple datasets on a single graph. Starting in the second column (column B), enter values for the horizontal (independent) axis on the first row of the worksheet. In like fashion, enter values for the vertical (dependent) axis on the second row. For multiple trials, enter the values on subsequent rows. For example, if you are setting a series of voltages in a circuit and then measuring the resulting currents, the voltages would be in row one and the currents in row two. If you changed the circuit components, reset the voltages, remeasured the currents and wish to compare the two trials, then the new set of currents would be in row three and so on. Each of these rows would have their identifying legend in column A with the numeric data starting in column B. Specifically, the legend text for the first data set would be in cell `$A$2` and the numeric values would be in cells `$B$2` through `$X$2` (where X is the final data column), for the second set the legend text would be in cell `$A$3` and the numeric values would be in cells `$B$3` through `$X$3`, etc.
2. Select/highlight all of the data (click the first cell, in the upper left corner, and drag the mouse over all of the cells used).
3. Select the Insert menu and choose Chart. Ordinarily you will use an **XY Scatter** chart. There are other options but this is the one you'll need in most cases. A simple Line chart is **not** appropriate in most cases. You might get a graph that “sort of” looks correct but the horizontal axis will simply represent the measurement sequence (first, second, third) rather than the value you set.
4. You can customize the appearance of the chart. In general, you can edit items by simply double-clicking on the item or by using a right-mouse click to bring up a property menu. This will allow you to add or alter gridlines, axes, etc. You can also stipulate variations such as using data smoothing, adding a trend line, etc. It is possible to change the axes to logarithmic or alter their range; and fonts, colors and a variety of secondary characteristics may be altered.
5. Once your chart is completed, you may wish to save the worksheet for future reference. To insert the chart into a lab report, select the chart by clicking on it, copy it to the clipboard (Ctrl+C), select the insertion point in the lab report, and paste (Ctrl+V).

6. In those odd instances where you need to reverse the dependent and independent axes such as a VI plot of a diode where currents are set and resulting voltages are measured, but you want the voltage on the horizontal, some spreadsheets have an axis swap function. If not, you'll need to swap the data ranges for the chart axes. For example, following the instructions above, your independent/horizontal axis is row one. The data are in cells \$B\$1 through \$X\$1. The dependent data are in cells \$B\$2 through \$X\$2. These ranges can be seen in the chart's Data Series or Data Range menu or dialog box. It will say something like: "X Values: =Sheet1!\$B\$1:\$F\$1" and "Y Values: =Sheet1!\$B\$2:\$F\$2". Simply swap the row numbers so that it says "X Values: =Sheet1!\$B\$2:\$F\$2" and "Y Values: =Sheet1!\$B\$1:\$F\$1".

7. Data smoothing can be useful to remove the "jaggyness" of some plots. For simple curves, a second degree B-Spline is suggested if you're using Open Office. For data that are expected to be linear, a trend line can be useful to better see the approximation.

Here is an example worksheet showing a plot of two resistors. The first plot is basic, the second uses smoothed data with a linear trend line:

